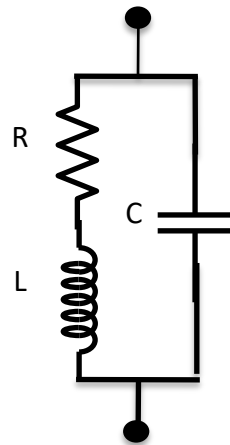





$$Z^2 = R^2 + (\omega L - 1/\omega C)^2$$




$$Z = (L/C - j(R/\omega C)) (R + j(\omega L - 1/\omega C))^{-1}$$

$$f_0 = (2\pi)^{-1} (LC)^{-1/2}$$

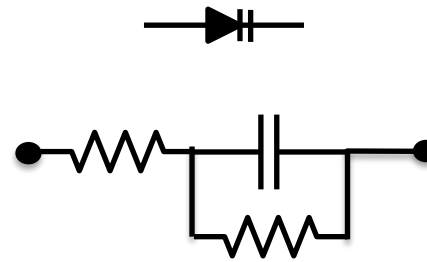


Varactor model
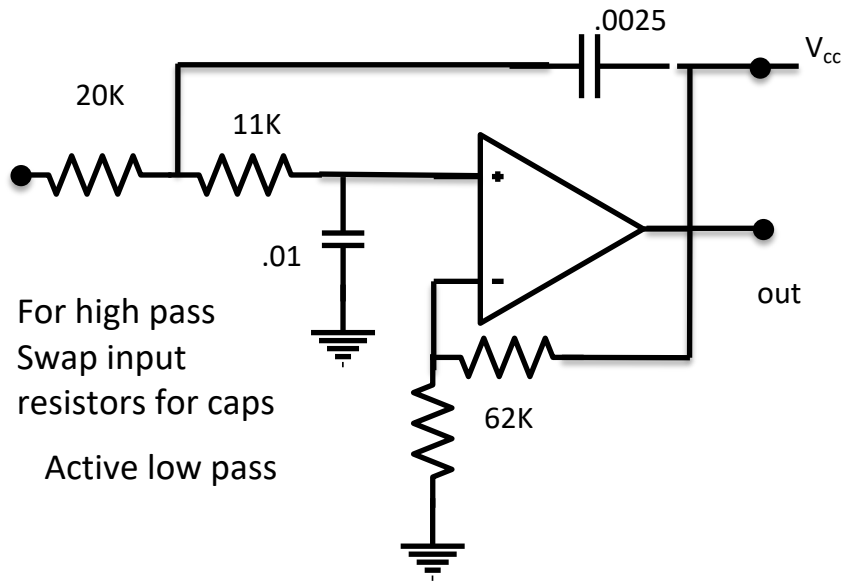
$$C_j = \frac{C_{j0}}{\sqrt{V_{on} - V_{revbias}}}$$




For high pass
Swap input
resistors for caps
Active low pass

Flat side transistor (L to R): E, B, C

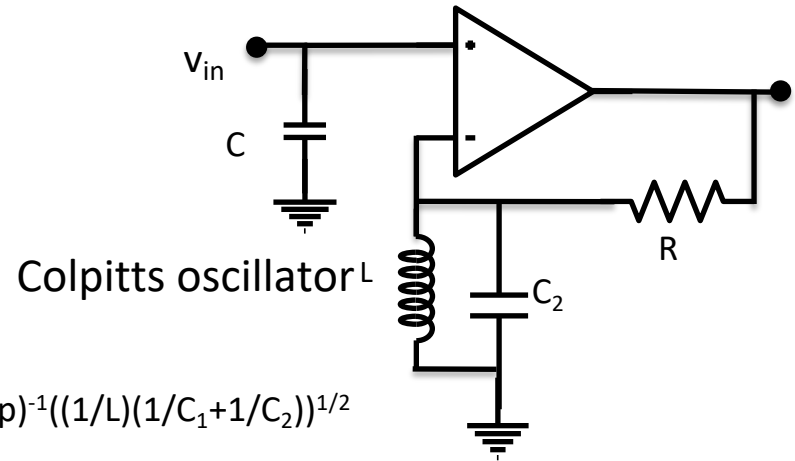

Colpitts oscillator
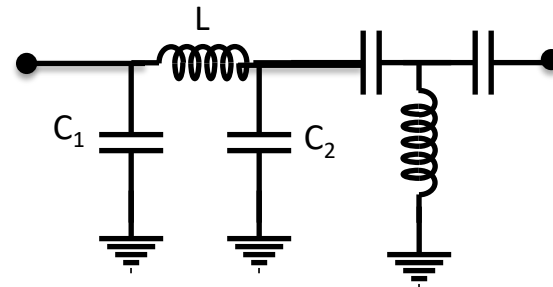
$$f = (2\pi)^{-1} ((1/L)(1/C_1 + 1/C_2))^{1/2}$$



π and T impedance matching