
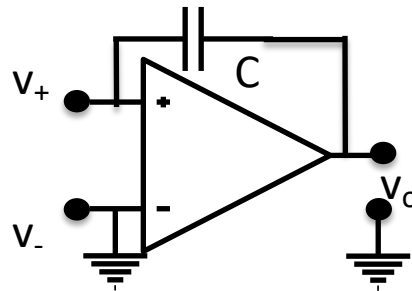



Ideal Amplifier

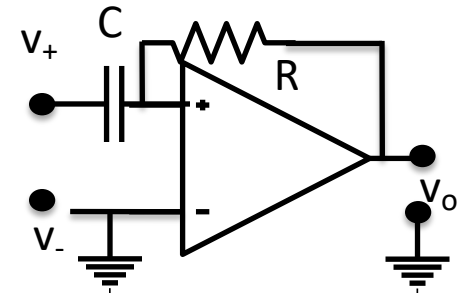


Integrator




Differentiator

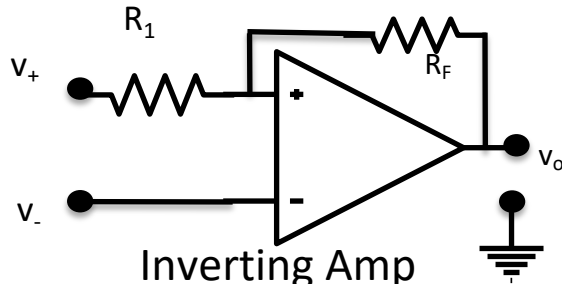


Inverting Amp

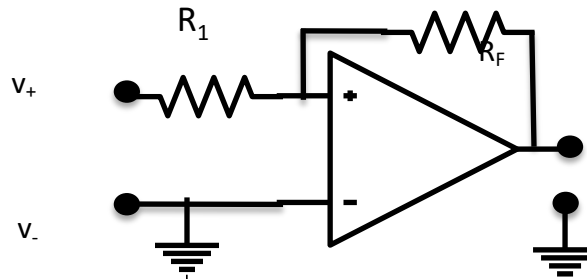


Non-inverting Amp

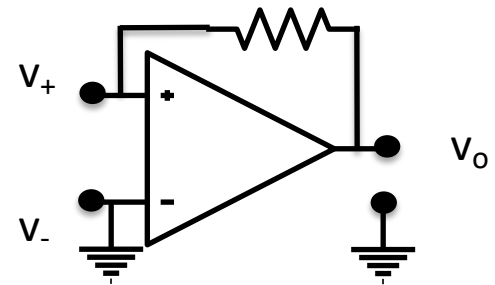


Follower as buffer

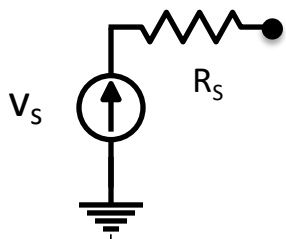

Bipolar source model

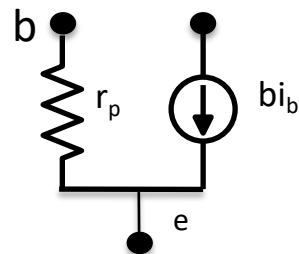

Simple bipolar model

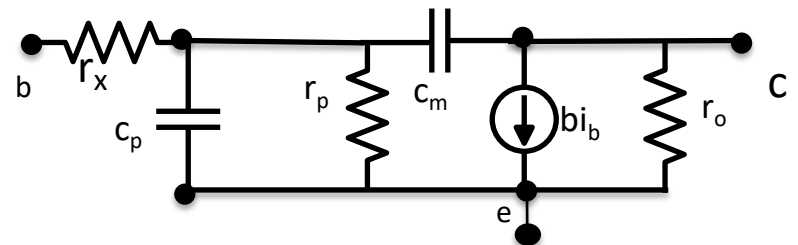

High frequency bipolar model (npn)