

# Electronics of Radio

Notes on David Rutledge's book

John Manferdelli  
johnmanferdelli@hotmail.com

# Basic concepts

- Potential difference ( $V, \phi$ ):  $\phi = \int_a^r E \cdot ds$ , energy per charge,  $1V = 1 J/s$
- Kirkoff 1:  $\sum_{loop} V_i = 0$  (Conservation of energy)
- Kirkoff node:  $\sum_{node} I_i = 0$  (Conservation of charge)
- $V(t) = V_p \cos(\omega t)$ ,  $\omega = 2\pi f$ ,  $I(t) = I_p \cos(\omega t)$ ,  $\omega = 2\pi f$
- Instantaneous power:  $P(t) = V(t)I(t) = V_p I_p \cos^2(\omega t)$
- Average power:  $P_a = \int_0^{1/f} V(t)I(t)dt = V_p I_p \int_0^{2\pi/\omega} \cos^2(\omega t)dt = \frac{V_p I_p}{2}$
- Band names:

Name	Frequency
VLF	3-30kHz
LW	20-300kHz
MW	300kHz-3MHz
HF	3MHz-30MHz
VHF	30-300MHz

Name	Frequency
UHF	300MHz-1GHz
uW	1-30GHz
milliW	30-300GHz
submilliF	>300GHz

# Signals

- Gain (G) expressed in decibels:  $G = 10 \log_{10}(P_{out}/P_{in})$
- Mixer:
  - $V(t) = \cos(\omega_1 t) \cos(\omega_2 t) = \frac{1}{2} [\cos(\omega_+ t) + \cos(\omega_- t)]$ ,  $\omega_+ = \omega_1 + \omega_2$ ,  $\omega_- = \omega_1 - \omega_2$
- Modulation

Name	Equation
AM	$V(t) = a(t)\cos(\omega_c t)$
FM	$V(t) = V_c \cos((\omega_c + a(t))t)$
FSK	$V(t) = V_c \cos(\omega_1 t)$ , if 1 $V(t) = V_c \cos(\omega_0 t)$ , if 0
PSK	$V(t) = +V_p \cos(\omega t)$ , if 1 $V(t) = -V_p \cos(\omega t)$ , if 0

# Resistors, capacitors, inductors

- Resistors

- Analytic model:  $IR = V$
- Energy dissipated:  $E = \int_{t_i}^{t_f} IV \, dt = \int_{t_i}^{t_f} I^2 R \, dt$

- Capacitors

- Analytic model:  $CV = q, C \frac{dV}{dt} = i$
- Capacitor Energy stored:  $E = \int_{t_i}^{t_f} CV \frac{dV}{dt} \, dt = \frac{1}{2} CV^2$

- Inductors


- Analytic model:  $V = L \frac{di}{dt}$
- Inductor Energy stored:  $E = \int_{t_i}^{t_f} IV \, dt = \int_{t_i}^{t_f} LI \frac{dI}{dt} \, dt = \frac{1}{2} LI^2$



Credit: Make Electronics
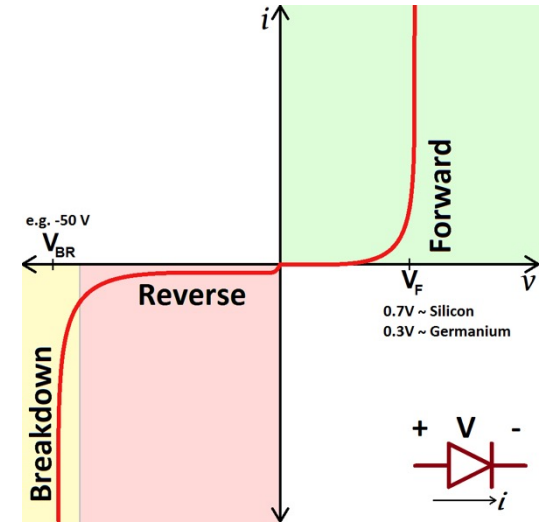
# Diodes, transformers

- Diodes
  - Devices that allow current to flow only in one direction
  - Silicon diodes, for example have, essentially infinite resistance if  $V_{ac} < 0$ , that is if the cathode is at a higher potential than the anode and very low resistance if  $V_{ac} > .7V$ .
  - The cathode is usually labelled with a band
- Transformers
  - AC only:  $\frac{N_2}{N_1} = \frac{V_2}{V_1}$



Credit: Make Electronics



# Simple circuit analysis with Kirchhoff



- $R_{eq}$  is the equivalent resistance, replacing the top left circuit with a single resistance.
- By Kirchhoff's node rule,  $i_1 = i_2 = i$ , so
- $\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2} = \frac{V_1}{R_{eq}}$  thus  $\frac{R_1}{R_{eq}} V_1 = V_1 - V_2$  and  $\frac{R_2}{R_{eq}} V_1 = V_2$ . Adding, we get  $\frac{R_1}{R_{eq}} V_1 + \frac{R_2}{R_{eq}} V_1 = V_1$ . Dividing by  $V_1$  and solving, we get  $R_1 + R_2 = R_{eq}$



- Again let  $R_{eq}$  is the equivalent resistance, replacing the bottom left circuit with a single resistance.
- By Kirchhoff's node rule,  $i_1 + i_2 = i$ , so
- $\frac{V_1}{R_1} + \frac{V_1}{R_2} = \frac{V_1}{R_{eq}}$ .
- Solving, we get.  $\frac{R_1 R_2}{R_1 + R_2} = R_{eq}$

- $C_{eq}$  is the equivalent capacitance, replacing the top right circuit with a single capacitor.
- By Kirchhoff's node rule,  $i_1 = i_2 = i$ , so
- $C_1 \frac{d(V_1 - V_2)}{dt} = C_2 \frac{d(V_2)}{dt} = C_{eq} \frac{dV_1}{dt}$
- $\frac{C_{eq}}{C_1} \frac{d(V_1)}{dt} = \frac{d(V_1 - V_2)}{dt}$  and  $\frac{C_{eq}}{C_2} \frac{d(V_1)}{dt} = \frac{d(V_2)}{dt}$
- Adding and cancelling the  $\frac{d(V_1)}{dt}$ , we get
- $\frac{C_{eq}}{C_1} + \frac{C_{eq}}{C_2} = 1$  and solving, we get.  $\frac{C_1 C_2}{C_1 + C_2} = C_{eq}$



- $C_{eq}$  is the equivalent capacitance, replacing the bottom right circuit with a single capacitor.
- By Kirchhoff's node rule,  $i_1 + i_2 = i$
- $C_{eq} \frac{dV_1}{dt} = C_1 \frac{dV_1}{dt} + C_2 \frac{dV_1}{dt}$ , so
- $C_{eq} = C_1 + C_2$



# Simple circuit analysis with Kirchhoff




- Let  $L_{eq}$  be the equivalent inductance, replacing the top left circuit with a single inductor.
- By Kirchhoff's node rule,  $i_1 = i_2 = i$ , so
- $L_{eq} \frac{di}{dt} = V_1$ ,  $L_1 \frac{di_1}{dt} = V_1 - V_2$ ,  $L_2 \frac{di_2}{dt} = V_2$
- $V_1 = L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$  and
- $L_{eq} = L_1 + L_2$



- Let  $L_{eq}$  be the equivalent inductance, replacing the bottom left circuit with a  $\frac{di}{dt} = \frac{V_1}{L_{eq}}$ ,  $\frac{di_1}{dt} = \frac{V_1}{L_1}$ ,  $\frac{di_2}{dt} = \frac{V_1}{L_2}$ , single inductor.
- By Kirchhoff's node rule,  $i_1 + i_2 = i$ , so
- $\frac{V_1}{L_{eq}} = \frac{V_1}{L_1} + \frac{V_1}{L_2}$  and
- $L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$

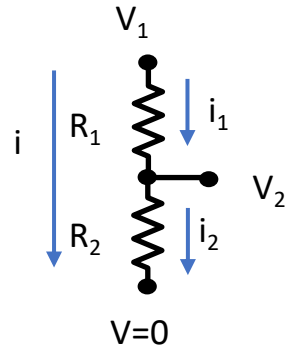- The circuit on the right, is useful and is called a *voltage divider*.
- $i = i_1 = i_2$  so  $\frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2}$ ,  $V_1 - V_2 = \frac{R_1}{R_2} V_2$
- Thus,  $V_1 = (1 + \frac{R_1}{R_2}) V_2$  and so
- $V_2 = \frac{R_2}{R_1 + R_2} V_1$



# RC/RL circuit analysis with Kirchhoff



- RC behavior: charging

- $V_0 - V_2 = i_1 R = V_R, i_1 = \frac{V_R}{R}$
- $i_2 = C \frac{dV_2}{dt}, V_C = V_2$
- $i_1 = i_2, V_C = V_0 - V_R$
- $\frac{V_R}{R} = C \frac{dV_C}{dt}, RC \frac{dV_C}{dt} = V_0 - V_C, \text{ or } RC \frac{dV_C}{dt} + V_C = V_0$
- Solution is  $V_C = V_0 - V_0 e^{-\frac{t}{RC}}$



- RL behavior: charging

- $V_0 - V_2 = i_1 R = V_R$
- $V_L = V_2 = L \frac{di_2}{dt}$
- $i_1 = i_2, V_R = V_0 - V_L, \text{ so } L \frac{d}{dt} \frac{V_0 - V_L}{R} = V_L$
- $\frac{L}{R} \frac{dV_L}{dt} + V_L = 0$
- Solution is  $V_L = V_0 e^{-\frac{Rt}{L}}$





# Phasors

- $V(t) = RI(t)$
- $V(t) = L\dot{I}(t)$
- $I(t) = C\dot{V}(t)$
- Suppose  $V(t) = A\cos(\omega t + \theta)$  and  $I(t) = B\cos(\omega t + \phi)$ . If  $\phi > \theta$ , we say the current leads the voltage.
- $V(t) = \text{Re}(e^{j(\omega t + \theta)})$ , and  $I(t) = \text{Re}(e^{j(\omega t + \phi)})$
- Now define  $V = Ae^{j\theta}$  and  $I = Be^{j\phi}$ , so  $|V| = A$ ,  $|I| = B$ ,  $\angle V = \theta$ , and  $\angle I = \phi$ .  $V$  and  $I$  are called phasors and do not include time. Note that  $V(t) = \text{Re}(Ve^{j\omega t})$  and  $I(t) = \text{Re}(Ie^{j\omega t})$ .
- Note that  $I = CVj\omega$ , for a capacitor and  $V = LIj\omega$ , for an inductor

# Circuit analysis and impedance

- Impedance unifies the “simple” ohms law with capacitance and inductance.
- $Z = R$ , for resistors,  $Z = j\omega L$ , for inductors and  $Z = \frac{1}{j\omega C}$ , for capacitors.
- In general,  $Z = R + jX$  and all the ohm like laws hold for resistors, capacitors and inductors .
  - $Z_{eq} = Z_1 + Z_2$  for two components with impedance  $Z_1, Z_2$  connected in series
  - $Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$  for two components with impedance  $Z_1, Z_2$  connected in parallel
- For example, for a resistor and capacitor in series has impedance  $Z = R + \frac{1}{j\omega C}$

# Phasors, impedance and power

- For the circuit on the right,  $Z = R + \frac{1}{j\omega C}$  is the impedance for the resistor and capacitor in series.
- The phasor  $I = \frac{V_0}{Z}$  and the phasor  $V = \frac{I}{j\omega C} = \frac{V_0}{1+j\omega RC}$
- Further,  $|I| = \frac{V_0}{|Z|}$ ,  $\angle I = \angle \frac{V_0}{|Z|}$  and  $|V| = \frac{|I|}{|j\omega C|} = \left| \frac{V_0}{1+j\omega RC} \right|$
- For phasors  $V, I$ , define the complex power as  $P = \frac{V\bar{I}}{2} = Z \frac{I\bar{I}}{2} = R \frac{|I|^2}{2} + jX \frac{|I|^2}{2}$ ; the first term is the real power, the second is called the *reactive* power.
- The average power is  $P_a = \text{Re}(P) = \text{Re}\left(\frac{V\bar{I}}{2}\right)$ . We define the reactive power as  $P_r = \text{Im}(P)$ .
- $P_r = \omega(E_L - E_C)$ , where  $E_L$  and  $E_C$  are respectively, the energy stored in the inductor and capacitor respectively.



# Q and phasors

- Consider the series resonance on the right.  $Z_{LCR} = R + j\left(\omega L - \frac{1}{\omega C}\right)$
- The phasor,  $I = \frac{V_0}{Z_{LCR}}$ , and the phasor  $V_R = \frac{V_0}{Z_{LCR}} Z_R$ , where  $Z_R = R$ .
- So  $V_R = \frac{RC\omega V_0}{RC\omega + j(LC\omega^2 - 1)}$ .
- $|V_R|$  is maximum when  $\omega^2 LC = 1$ . Put  $\omega_0 = \frac{1}{\sqrt{LC}}$ . When  $\omega = \omega_0$ ,  $|V_R| = V_R = V_0$ .
- $|V_R| = \frac{V_0}{\sqrt{2}}$ , when  $X = R$ . Note that the power through R when  $X = R$  is half the power through R when  $X = 0$  or  $\omega = \omega_0$ .
- Let the frequencies where  $R = \pm X$  be denoted  $\omega_u$  and  $\omega_l$ , where  $\omega_u > \omega_l$ .
- We define  $Q = \frac{X}{R} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR}$ .
- Solving for  $\omega_u$  and  $\omega_l$ , we get  $\frac{L\omega_u}{\omega_0} - \frac{\omega_0}{C\omega_u} = R$  and  $\frac{L\omega_l}{\omega_0} - \frac{\omega_0}{C\omega_l} = -R$ , or, in terms of  $Q$ ,
- $\frac{\omega_u}{\omega_0} - \frac{\omega_0}{\omega_u} = \frac{1}{Q}$  and  $\frac{\omega_l}{\omega_0} - \frac{\omega_0}{\omega_l} = -\frac{1}{Q}$ . In fact,  $\omega_0 = \sqrt{\omega_u \omega_l}$ , and so  $\frac{\omega_u}{\omega_0} - \frac{\omega_l}{\omega_0} = \frac{1}{Q}$ .
- Thus  $Q = \frac{\omega_0}{\omega_u - \omega_l} = \frac{\omega_0}{\Delta\omega}$
- From the definition of  $P_a$ , earlier,  $Q = \omega_0 \frac{E}{P_a}$ , where  $E$  is the total energy stored in  $L$  and  $C$ , which is in turn the peak  $E_L$  and peak  $E_C$  at resonance.




# Phasors, impedance and power

- For the circuit on the right,  $Z = R + \frac{1}{j\omega C}$  is the impedance for the resistor and capacitor in series.
- The phasor  $I = \frac{V_0}{Z}$  and the phasor  $V = \frac{I}{j\omega C} = \frac{V_0}{1+j\omega RC}$
- Further,  $|I| = \frac{V_0}{|Z|}$ ,  $\angle I = \angle \frac{V_0}{|Z|}$  and  $|V| = \frac{|I|}{|j\omega C|} = \left| \frac{V_0}{1+j\omega RC} \right|$
- For phasors  $V, I$ , define the complex power as  $P = \frac{V\bar{I}}{2} = Z \frac{I\bar{I}}{2} = R \frac{|I|^2}{2} + jX \frac{|I|^2}{2}$ ; the first term is the real power, the second is called the *reactive power*.
- The average power is  $P_a = \text{Re}(P) = \text{Re}\left(\frac{V\bar{I}}{2}\right)$ . We define the reactive power as  $P_r = \text{Im}(P)$ .
- $P_r = \omega(E_L - E_C)$ , where  $E_L$  and  $E_C$  are respectively, the energy stored in the inductor and capacitor respectively.



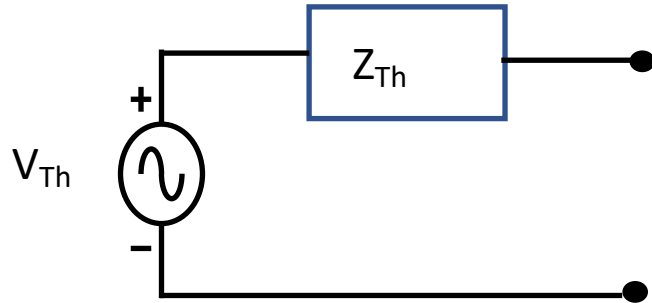
# Thevenin and Norton

- Thevenin: Any combination of linear sources and passive elements terminating in two terminals is equivalent to a pure voltage source in series with an impedance



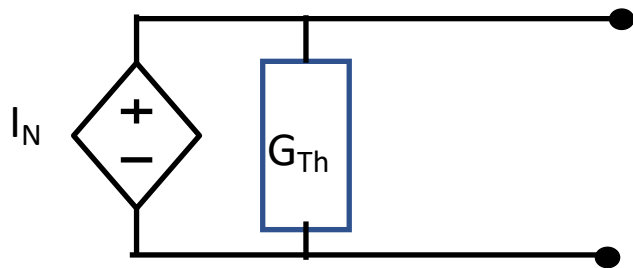
- Norton: Any combination of linear sources and passive elements terminating in two terminals is equivalent to a pure current source in parallel with a conductance



- Similar theorems for two terminal input and output devices (with transfer function)

# Thevenin and Norton

- We can use lookback resistance to calculate the Thevenin equivalent resistance and ideal source.
- To find the lookback resistance, short the source and apply the usual laws.
  - Here  $R_s = R_1 || R_2$
- To find the new ideal source, notice  $R_1$  and  $R_2$  form a voltage divider.
  - The new source voltage is  $\frac{V_0 R_2}{R_1 + R_2}$

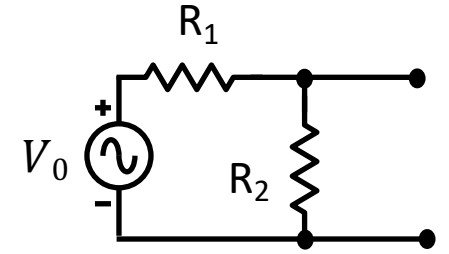

Is equivalent to



# Exercise 1: Resistors

1. Consider (A). Find the formula for power in the load. Find the  $R_l$  that maximizes the power to the load.


- $V_l = \frac{R_l}{R_s + R_l} V_0, I_l = \frac{V_0}{R_s + R_l}.$
- $P_l = V_l I_l = \frac{R_l}{(R_s + R_l)^2} V_0^2,$  which is maximum when  $R_l = R_s$

2. Find the Thevenin and Norton parameters fore (B).

- $V_{Th} = \frac{R_3}{R_1 + R_3} V_0$
- $R_{Th} = R_2 + R_1 || R_3$

3. Find the Thevenin and Norton parameters fore (C).


- $V_{Th} = \frac{R_3}{R_2 + R_3} V_0$
- $R_{Th} = R_2 || R_3$

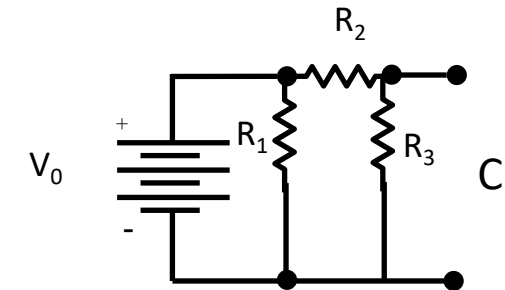




# Exercise 3: Capacitors

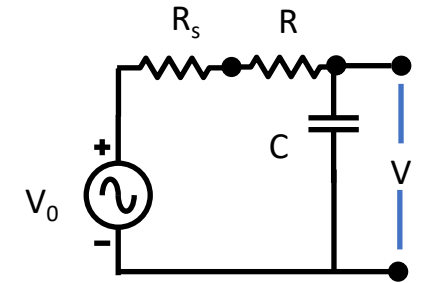1. In the circuit on the right,  $V_0$  is a 2 volt pp ideal square wave source of frequency 20Hz,  $R_S = 50\Omega$ ,  $R = 300k\Omega$  and  $C = 10\text{ nF}$ . Period is 50 *millisec*
2. What is the voltage,  $V$ , at the output? The scope has an input resistance of  $1M\Omega$ .
  - About a volt at peak
3. Let  $t_2$ , the time to discharge to 0V. Calculate  $\tau$  and  $t_2$ .
  - $\tau = 3 \times 10^5 \times 10^{-8} \text{ sec} = 3 \text{ millisec}$
  - $t_{12} \approx 1.5\text{ms}$
4. Capacitance on the scope prevents the delay from being 0. Measure the new  $t_2$  with these changes.
5. Given  $C_0$  and  $C_p$  and  $R_p$ .
  - $C_0 = 100\text{pf}/m$ ,  $C_o = 50\text{pF}$ ,  $C_p = 10\text{pF}$
6. Now calculate the new  $t_{12}$ .
  - $\tau = 6\mu\text{-sec}$




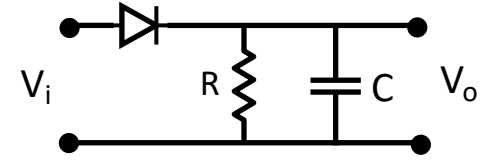
# Exercise 4: Diode detectors

- For AM,  $V(t) = V_c \cos(\omega_c t) + a(t) \cos(\omega_c t)$ , Define the modulation depth  $m = \frac{a_p}{V_c}$
- In circuit on the right,  $R = 3k\Omega$ ,  $C = 10\text{ nF}$
- Set function generator for  $f_c = 1\text{MHz}$ ,  $V_{c,pp} = 5\text{V}$ ,  $f_m = 1\text{kHz}$ ,  $m = .7$ 
  1. Calculate  $\tau$  for the RC circuit.  $\tau \ll a(t)$
  2. Compare the max voltage of the AM signal to the max of  $V_0$ .  $\tau \gg \frac{c}{f_c}$
  3. What happens when we make  $m = 1.0$


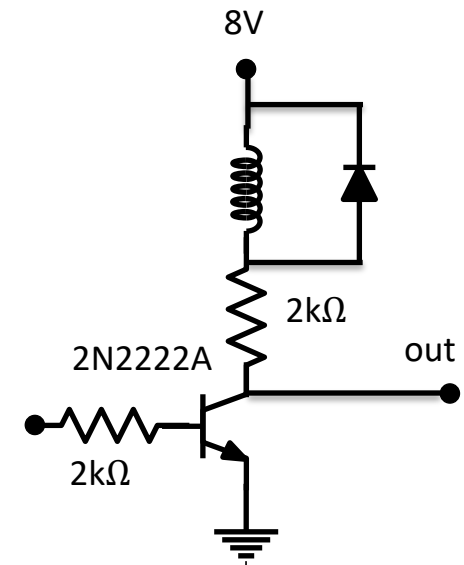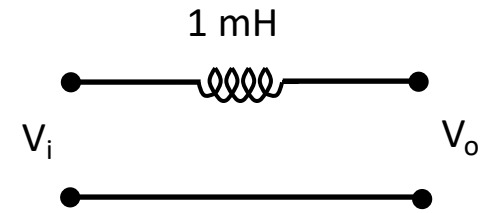
# Exercise 5: Inductors

- Set function generator for 5V  $V_{pp}$ , 1kHz. Connect a 50Ω load
  1. Observe square wave with rounded corners, measure the time,  $t_2$  to decay to 0
  2. Calculate pp inductor current and the expected delay,  $t_2$
  3. Use 2 scope channels: one at input, one at output






# Exercise 6: Diodes and snubbers

x

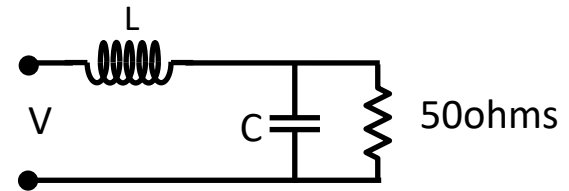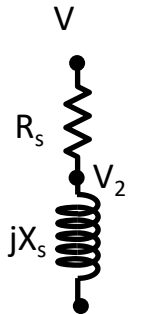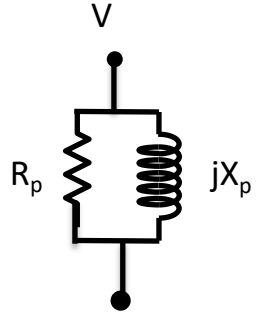
# Exercise 7: Parallel to Series conversion

- For series:  $Z_s = R_s + j\omega L$ ,  $Q_s = \frac{\omega L}{R_s}$
- For parallel:  $\frac{1}{Z_p} = \frac{1}{R_p} + \frac{1}{j\omega L}$ , so  $Z_p = \frac{j\omega L R_p}{R_p + j\omega L}$  and  $Q_p = \frac{R_p}{\omega L}$



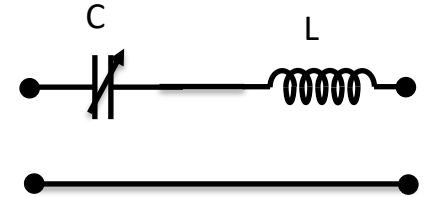
# Exercise 8: Series resonance

- For the circuit on the right,  $C = 8 - 50\text{pF}$ ,  $L = 15\mu\text{H}$  forming a bandpass filter.
- If  $C = 35\text{pF}$ , the resonant frequency is  $\omega = \frac{1}{\sqrt{35 \times 10^{-12} \times 15 \times 10^{-6}}} = \frac{10^9}{\sqrt{525}} \approx 43.6$ , so the resonant frequency is  $\frac{43.6}{2\pi} \approx 6.9\text{MHz}$
- Tune the resonant frequency to  $7\text{MHz}$  and find  $f_u$ ,  $f_l$  and  $\Delta f$  and thus  $Q$ .
- Compute what these values should be



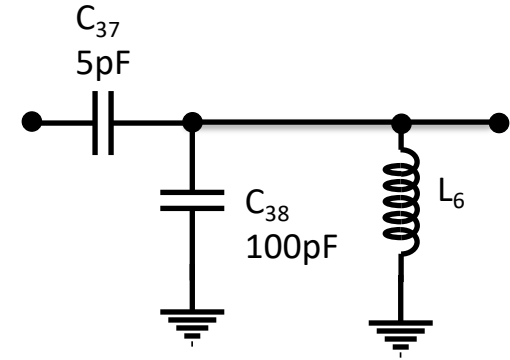
# Exercise 9: Parallel resonance

- $L = A_l N^2$ ,  $A_l = 4 \frac{nH}{turn^2}$  for T37-2 core so for 28 turns,  $L_6 = 3.1\mu H$
- 1. Again, find the resonant frequency, the frequencies corresponding to a 3db fall off, the bandwidth and the Q of this circuit. This circuit is in the transmit oscillator



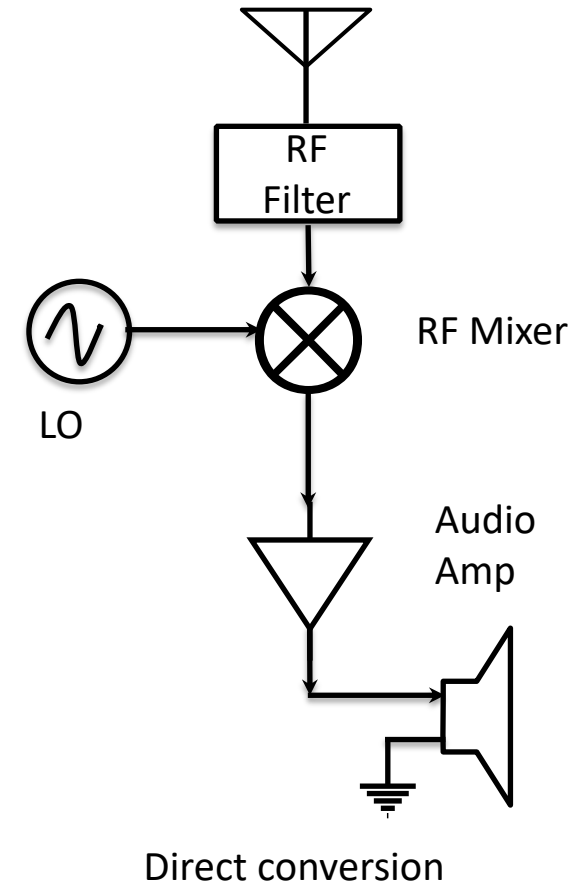
# Direct conversion and superhet receivers

- Image frequency
  - $\omega_{rf} = \omega_{LO} - \omega_a$
  - $\omega_i = \omega_{LO} + \omega_a$
- Superheterodyne designs
  - $\omega_{rf} = \omega_{IF} + \omega_{VFO}$
  - $\omega_{vi} = \omega_{IF} - \omega_{VFO}$
  - $\omega_{IF} = \omega_{BFO} - \omega_a$
  - $\omega_{bi} = \omega_{BFO} + \omega_a$
  - $\omega_{usb} = \omega_{VFO} + \omega_{BFO} + \omega_a$
  - $\omega_{lsb} = \omega_{VFO} + \omega_{BFO} - \omega_a$






# Norcal 40A

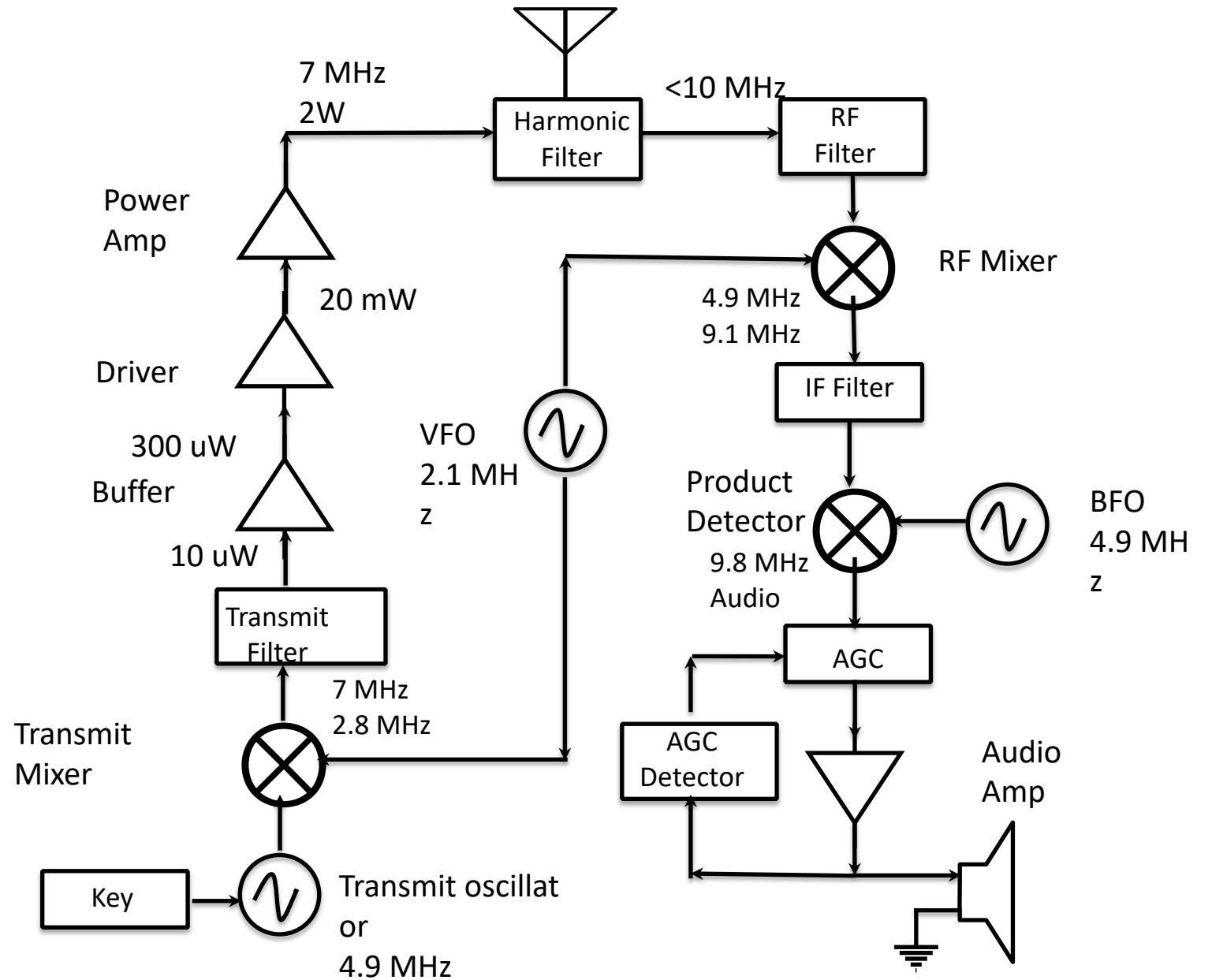

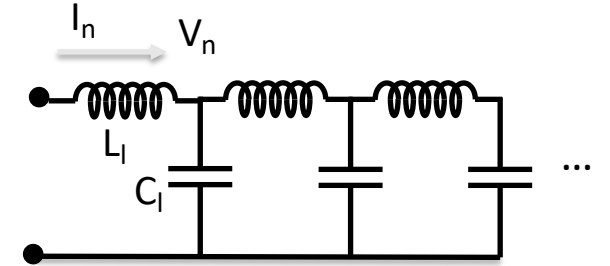
# Transmission Lines

- $V_{n+1} - V_n = -L_l \frac{\partial I_{n+1}}{\partial t}, L = \frac{L_l}{l}$
- $I_{n+1} - I_n = -C_l \frac{\partial V_n}{\partial t}, C = \frac{C_l}{l}$
- $\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2}$  and  $\frac{\partial^2 I}{\partial z^2} = LC \frac{\partial^2 I}{\partial t^2}$
- Solution is  $V(z - vt), v = \frac{1}{\sqrt{LC}}$ , for forward wave
- $V' = vLI', \frac{V}{I} = \sqrt{\frac{L}{C}}, Z_0 = \sqrt{\frac{L}{C}}$
- Another solution is  $V(z + vt), v = \frac{1}{\sqrt{LC}}$ , for reverse wave
- $Z_0 = \frac{V_+}{I_+}, -Z_0 = \frac{V_-}{I_-}, V = V_+ + V_-$
- $P_+(t) = \frac{V_+^2}{Z_0}, P_-(t) = -\frac{V_-^2}{Z_0}$
- $\rho = \frac{V_-}{V_+}, Z = \frac{V}{I} = \frac{V_+ + V_-}{I_+ + I_-} = \frac{V_+}{I_+} \frac{1 + \frac{V_-}{V_+}}{1 + \frac{I_-}{I_+}} = Z_0 \frac{1 + \rho}{1 - \rho}$
- $\rho = \frac{Z - Z_0}{Z + Z_0}$
- $\rho_i = \frac{i_-}{i_+} = -\rho$



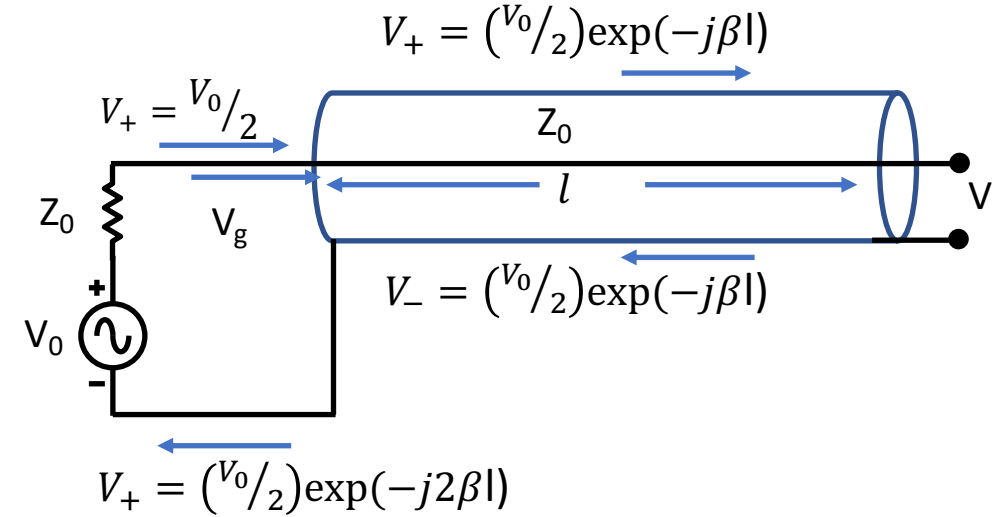
# Transmission Lines - continued

- Phasor:  $V(z - vt) = A \cos(\omega t - \beta z)$
- $\frac{dV}{dz} = -ZI, \frac{dI}{dt} = -YV'$
- $jk = \alpha + \beta j, jk = \sqrt{ZY}, Z_0 = \sqrt{\frac{Z}{Y}}$
- $jk = \sqrt{(j\omega L + R)(j\omega C + G)}, Z_0 = \sqrt{\frac{(j\omega L + R)}{(j\omega C + G)}}$
- $\alpha = \sqrt{\frac{\omega RC}{2}}, v = \sqrt{\frac{2\omega}{R}}$



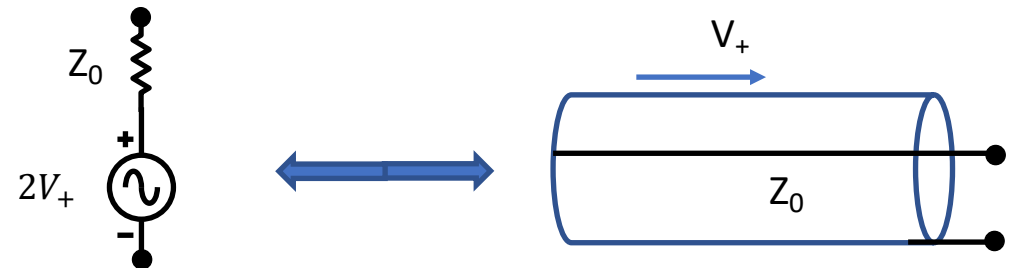
## Power

- $\tau = \frac{V}{V_+} = 1 + \rho = \frac{2Z}{Z + Z_0}, V = 2V_+$
- Lookback resistance is  $R_s = Z_0$
- $P_+ = \frac{V_+^2}{2Z_0} = \frac{V_0^2}{8Z_0}$ , This is the total available power



# Exercise 10: Coax

- Use  $50\Omega$  scope probe

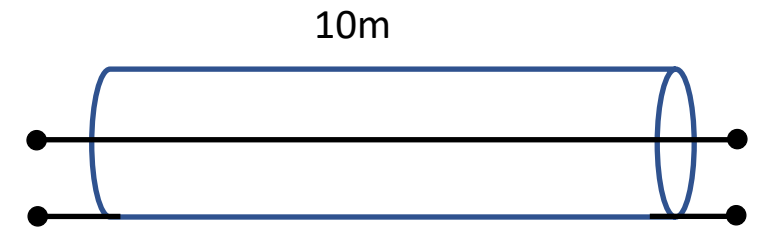


# Exercise 11: Waves

- Use 50 $\Omega$  scope probe


# Exercise 12: Resonance

- *RG58U* has a capacitance of about  $100 \text{ pF/m}$
- Let  $\alpha$  be the attenuation constant and  $\beta$  be the phase
- Derive an expression for  $|\frac{V_g}{V}|$  and use it to calculate  $\alpha$
- Find the wave velocity by calculating the resonant frequency and noting the time delay with a scope on the input and output
- Find, as usual,  $f_u$ ,  $f_u$ , and  $Q$ .
- Confirm  $Q = \frac{\alpha}{2\beta}$

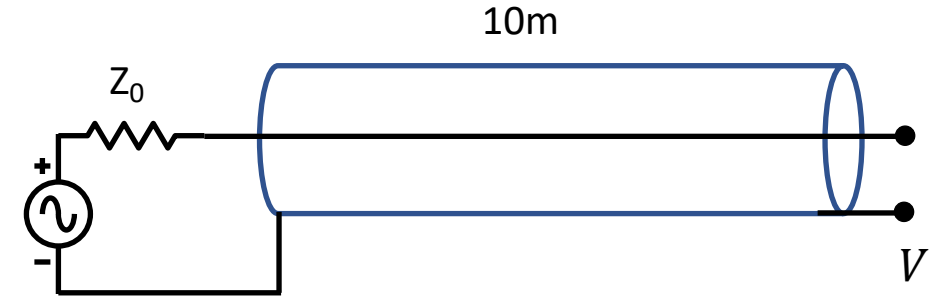


# Filters


Low pass

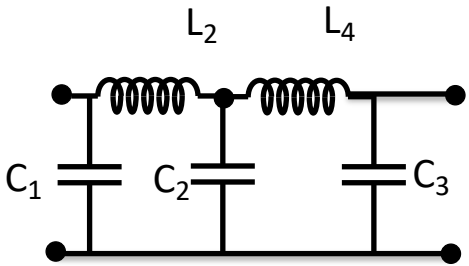


High pass

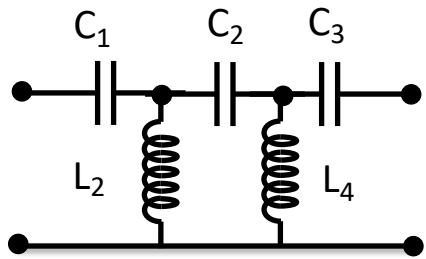


7 MHz bandpass

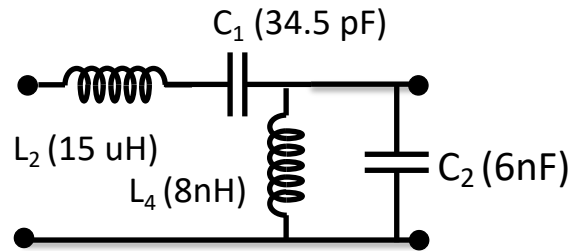

- Filters

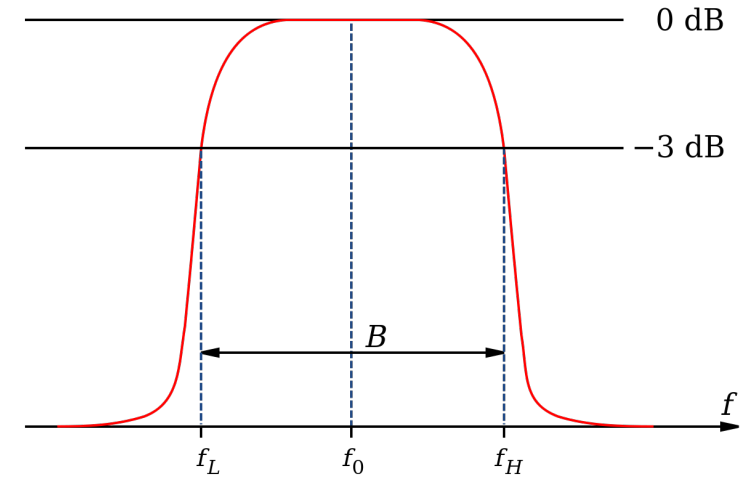


Bandpass - Wikipedia

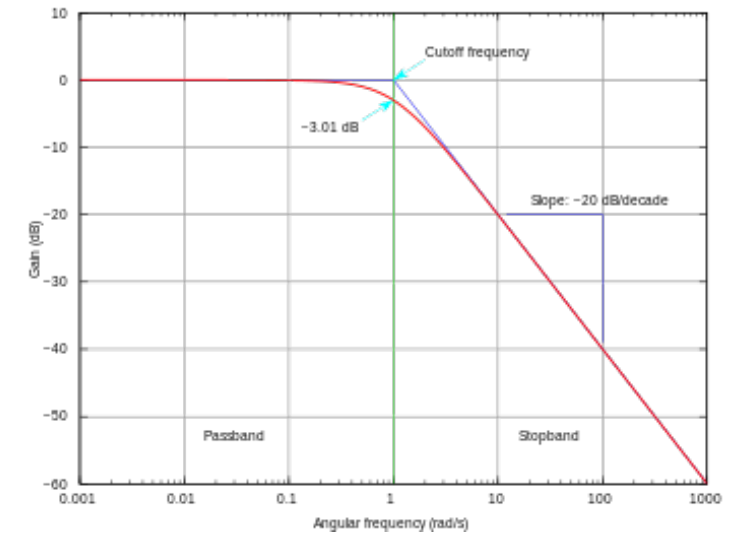

Lowpass - Wikipedia

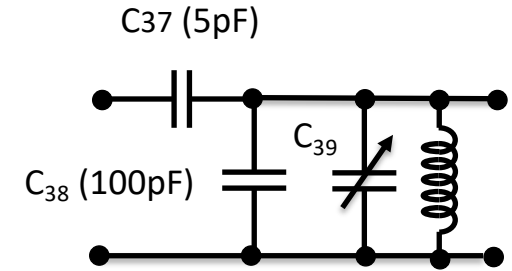
# Norcal transmit bandpass filter

- $C_{39} = 50\text{pF}$ ,
- $L_6$  is 36 turns #28 on T37-2 which has  $A_l = 4 \frac{\text{nH}}{\text{turn}^2}$
- $L_6 = A_l \cdot 36^2 = 3.1\mu\text{H}$
- $Z_2 = -\frac{j}{(C_{38}+C_{39})\omega_o}$ ,  $Z_3 = jL_6\omega_o$ ,  $Z_1 = \frac{j}{C_{37}\omega_o}$
- $Z_{2,3-eq} = \frac{jL_6\omega_o}{L_6(C_{38}+C_{39})\omega_o^2 - 1}$   $L_6$
- Resonance is when  $Z_{2,3-eq} \rightarrow \infty$ ,  $\omega_o^2 = \frac{1}{(C_{38}+C_{39})L_6} \approx \frac{10^{18}}{465}$ , when almost all the voltage drop is across  $Z_{2,3-eq}$   $\omega_o = \frac{10^9}{\sqrt{465}} \approx 50.8 \times 10^6$ ,  $f_0 = \frac{\omega_o}{2\pi} \approx 7.1 \text{ MHz}$
- Q of filter is:  $Q_s = \frac{X_s}{R_s}$ .  $R_s$  comes from the other components and must be measured
- Note that  $Z_{2,3-eq}$  is small for the other modulation product






# Norcal RF Filter

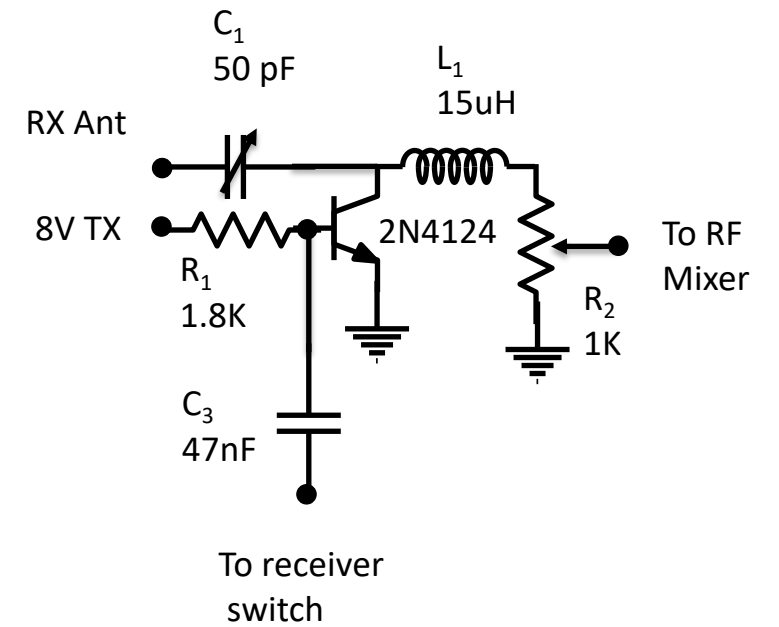


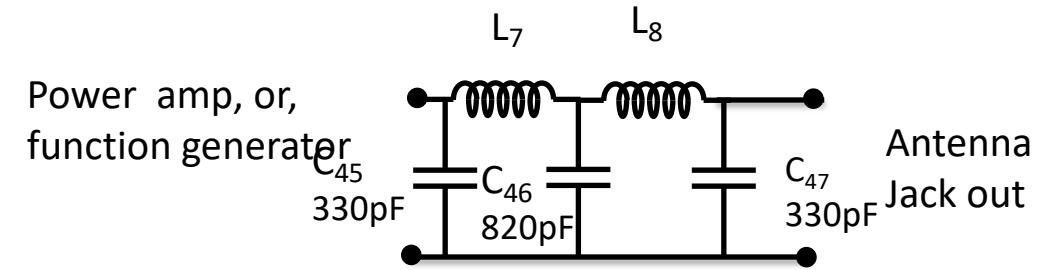
# Exercise 13: Norcal Harmonic Filter

- $L_7$ ,  $L_8$  use T37-2 core, 18 turns, 1.3uH
- Compare loss at 7MHz and 14MHz


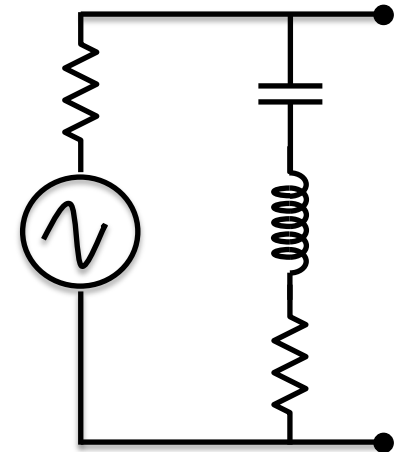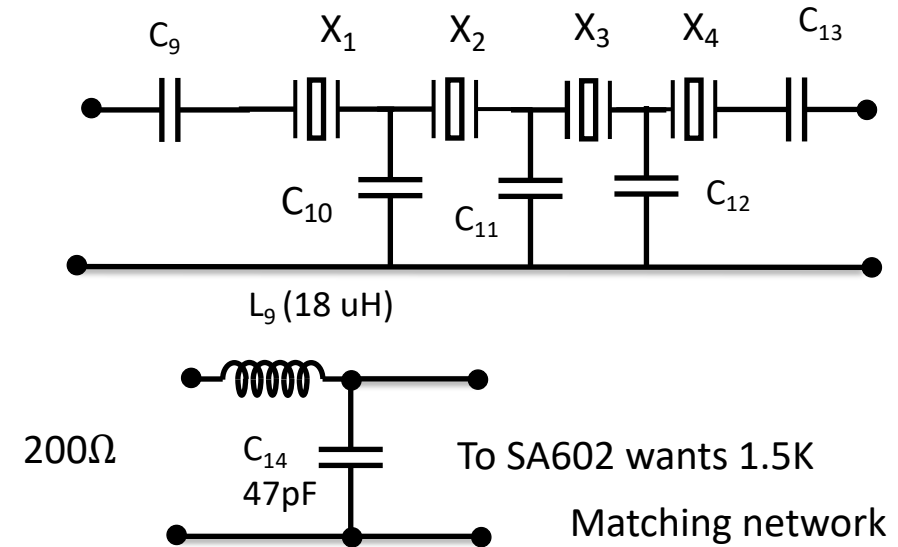
# Exercise 14: Norcal IF Cohn Filter

- $X_1$  through  $X_4$  are 4.91 MHz
- $C_{10}$ ,  $C_{11}$ ,  $C_{12}$  are 270 pF
- Set function generator to 50mV<sub>pp</sub> from function generator
- Calculate R and X for filter




Equivalent circuit for  
crystal and generator

# Transformers

- $V_s = \frac{N_s}{N_p} V_p$


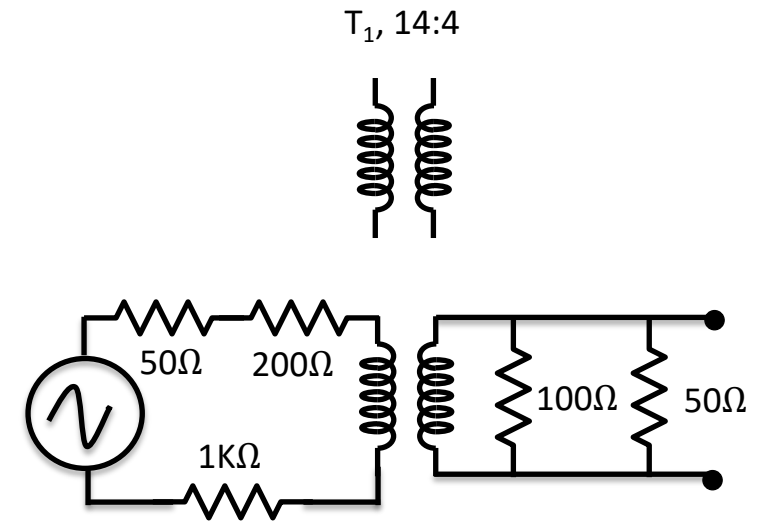
# Exercise 15: Norcal Driver Transformers

- $T_1$  is driver matcher uses FT 37-43
  1. Measure the output  $V$ .
  2. Calculate  $V$
  3. Measure the 3dB cutoff,  $f_c$ .
  4. Use  $f_c$  to calculate  $A_i$


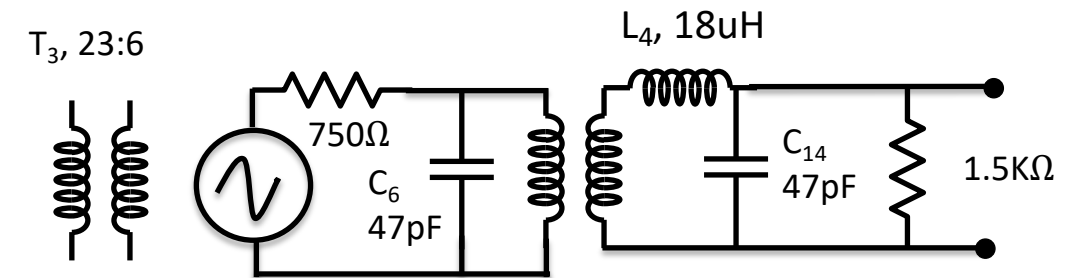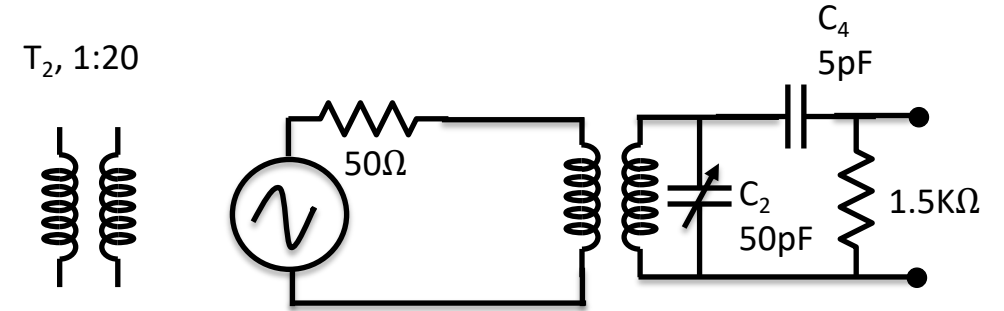
# Exercise 16: Norcal Tuned Transformers

- $T_2, T_3$  are IF matchers using FT 37-61
- .5Vpp sine at 7MHz
- 1. Measure 3dB bandwidth
- 2. Find  $P/P_+$



# Acoustics

- Section of air of length  $l$ ,  $U$  is average velocity,  $P$  is the pressure
- $\frac{\partial P}{\partial z} l = -\rho l \frac{\partial U}{\partial t}$
- $\frac{dl}{dt} = l \frac{\partial U}{\partial z}$
- $PV^\gamma = C$
- $\frac{\partial^2 P}{\partial t^2} = \frac{\gamma P}{\rho} \frac{\partial^2 P}{\partial x^2}$
- $v = \sqrt{\frac{\gamma P}{\rho}} = 332 \frac{m}{s}$
- $SWR = \frac{\lambda^2}{2\pi A}$ ,  $A$  is the area of the tube

Sound	L <sub>p</sub>	Power density
rustling leaves	10dB	1pW/m <sup>2</sup>
broadcast studio	20dB	1pW/m <sup>2</sup>
classroom	50dB	10nW/m <sup>2</sup>
heavy truck	90dB	1nW/m <sup>2</sup>
Shout at 1m	100dB	10mW/m <sup>2</sup>
jackhammer	110db	100mW/m <sup>2</sup>
jet takeoff at 50m	120dB	1W/m <sup>2</sup>

# Exercise 17: Tuned Speaker

- Connect speaker to function generator 600Hz, 25mVrms.
  1. Sound peaks at resonance. Find resonant frequency  $L_p$ .
  2. Measure  $f_l$ ,  $f_u$  by noting the 3dB loss. Calculate Q.
  3. Use voltmeter to find resonance with speaker (nominally 8ohm) to calculate impedance
  4. Calculate the resonant frequency from a transmission line equivalent circuit.





# Exercise 18: Acoustic Standing Wave


- $x$
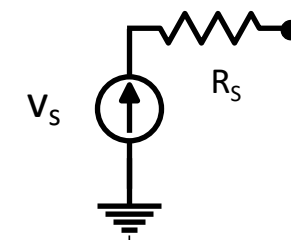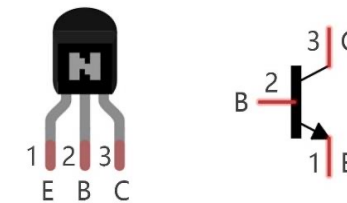
# Bipolar Transistors

- NPN, PNP types
- Model
  - Conducts when  $V_{be} > .7V$
  - $i_c = \beta i_b$
  - $i_c = \alpha i_e$
  - $\beta = \frac{\alpha}{1-\alpha}$
  - $\beta \sim 100$
- Switch
  - $G_S = \frac{i_b}{15mV}$
  - $R_S = 2\Omega$



Bipolar source model

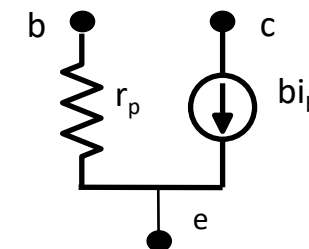

Bipolar equivalent circuit

# Blank


# BJT common emitter amplifier



Common emitter amp

- Here's how to design a common emitter amplifier. We use a 2n3904 transistor with  $\beta=150$ . This circuit will work! Build it.
1. Pick the supply voltage  $V_{cc}=12V$ .
  2. Choose a gain (amplification factor),  $A = 5$ .
  3. Choose the "Q point" of the conducting transistor (4mA).
  4.  $V_{cc} = (i_c \cdot R_C) + V_{ce} + i_e R_E \sim i_e \cdot (R_C + R_E) + V_{ce}$  with  $i_c=4mA$ . We get  $(R_C + R_E) = (V_{cc} - V_{ce})/(4mA) = 1.75 k\Omega$ .
  5. Since  $A = 5$  and  $A = R_C/R_E$ ,  $R_C = 5 R_E$  so  $R_E \sim 270 \Omega$  (this is a standard resistor value) and  $R_C = 1.5k\Omega$ .


# BJT common emitter amplifier continued

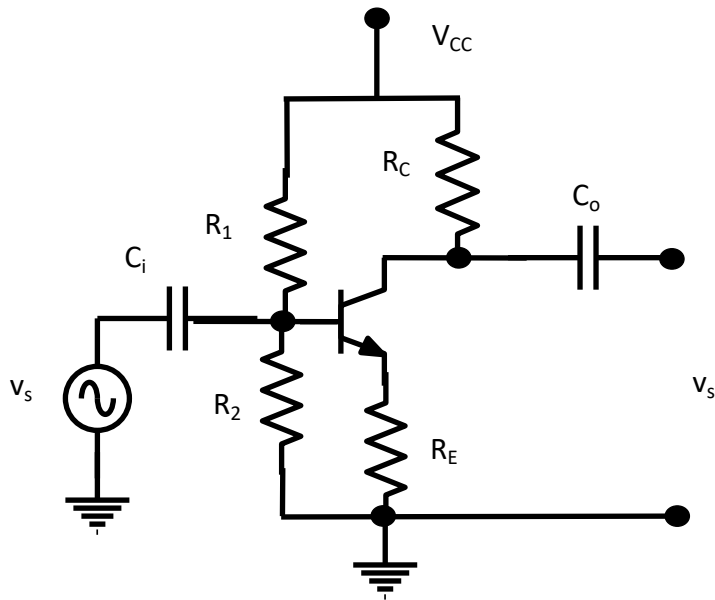

Common emitter amp

6.  $i_b = 4\text{mA}/\beta = 27 \mu\text{A}$ .
7. Since  $V_{be}$  must be greater than .7V throughout the input signal range, we want the voltage across  $R_2$  to satisfy  $V_{be} + i_c R_E = 1.8\text{V}$ .
8. We insert a voltage divider consisting of  $R_1$  and  $R_2$ , so that  $R_1 = (12 - 1.8)/270 \mu\text{A} \sim 39 \text{ k}\Omega$ .
9.  $C_o$  and  $C_i$  are picked to offer small resistance to the frequency range we're interested in and  $C_o = C_i = 5 \mu\text{F}$ .
- I haven't explained why we want  $R_E$  but it provides thermal stability for the transistor over the range we care about. The fact that  $A = R_C/R_E$  can be calculated using Kirchhoff's laws.

# BJT common collector amplifier

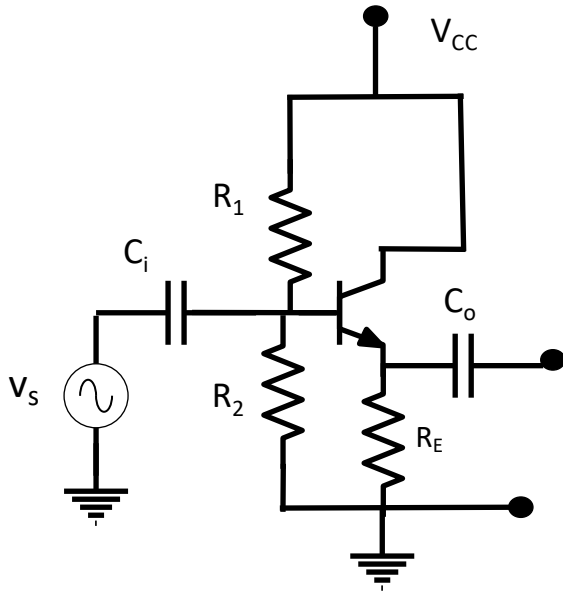


Common collector amp (Emitter Follower)

Common collector amp

1.  $\beta = 150, A_V = 1, V_{CC} = 12V$
2. Q-pt:  $i_{ce} = 5mA, V_{ce,q} = 6V$  (rule of thumb),  $v_{be} = .7V$ .
3.  $i_{R_1 \rightarrow R_2} = 10i_b$  (ROT),  $V_{ce} = v_{be} + i_{ce,q}R_E, R_E = 1.2k\Omega, i_b = \frac{V_{ce,q}}{\beta} = 33\mu A$
4.  $V_{R_2} = V_{be} + i_C R_E = 6.7V, V_{R_1} = 5.3V$
5.  $R_2 = \frac{6.7}{330\mu A} = 20k\Omega, R_1 = \frac{5.3}{330\mu A} = 16k\Omega$
6.  $Z_{in} = R_1 || R_2 || (\beta + 1)R_E, R_{in} = 50\Omega, Z_{out} = 5\Omega$

# Blank

# BJT common base amplifier

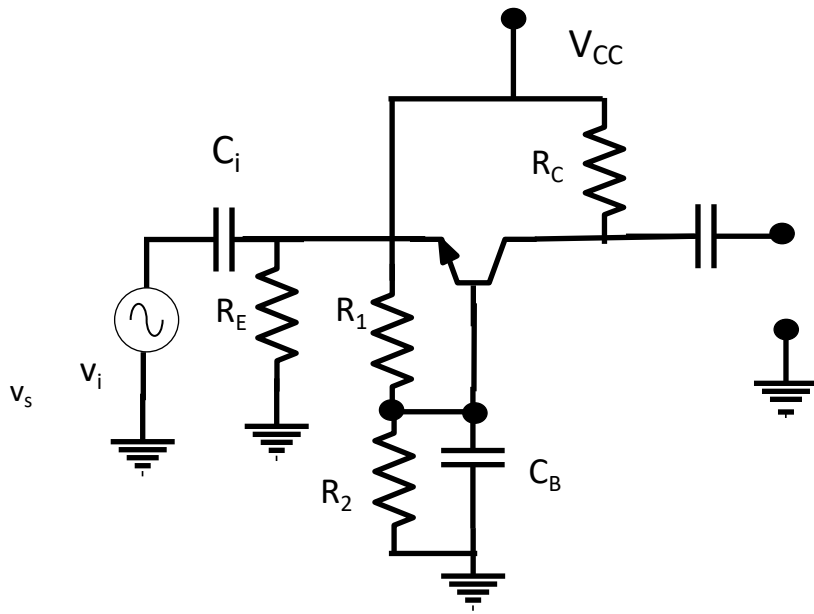

- $A_I = \frac{i_C}{i_E} = \frac{\beta}{\beta+1}$ ,  $A_V = \frac{R_C || R_L}{r_e}$ ,  $Z_{out} \approx R_C$
- 1.  $V_{CC} = 12V$ ,  $V_{be} = .7V$ ,  $R_E = 50\Omega$ ,  $R_L = 1k\Omega$ ,  $i_{ce,q} = 5mA$ ,  $V_{ce,q} = 6V$
- 2.  $i_b = \frac{i_{ce,q}}{\beta} = 33\mu A$ ,  $i_{R_1 \rightarrow R_2} = 10 i_b = 330\mu A$  (ROT)
- 3.  $V_{R_2} = V_{be} + i_C R_E = 6.7V$ ,  $V_{R_1} = 5.3V$
- 4.  $R_1 = \frac{5.3}{330\mu A} = 16k\Omega$ ,  $R_C = \frac{V_{CC} - i_{C,Q} R_E - V_{ce,Q}}{i_{C,Q}} = 1.35k\Omega$
- 5.  $A_V = \frac{R_C || R_L}{\frac{26}{i_e}} = 115$


Common base amp




# Blank
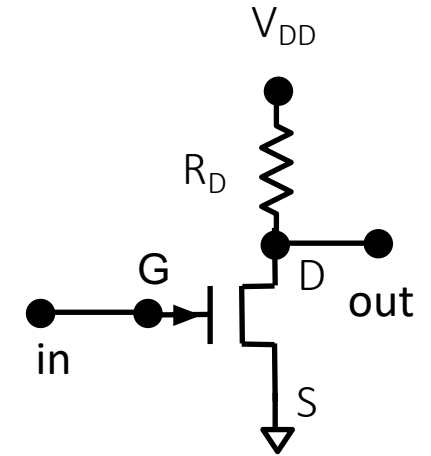
# JFETs

- JFET circuit model:  $I_{ds} = V_{ds}(\frac{2I_{dss}}{V_c^2})(V_{gs} - V_c - \frac{V_{ds}}{2})$
- $g_m = \frac{\Delta i_{ds}}{\Delta v_{gs}}$
- For circuit on right,  $g_m \Delta v_{gs} = \Delta i_{ds}$  and  $R_D \Delta i_{ds} = V_{out}$ , so  $-g_m R_D \Delta v_{gs} = V_{out}$
- Similar model for MOSFETs
- Op amp:  $V_{out} = A_{OL}(V_+ - V_-)$ , input resistance is very high



# JFET common source amplifier

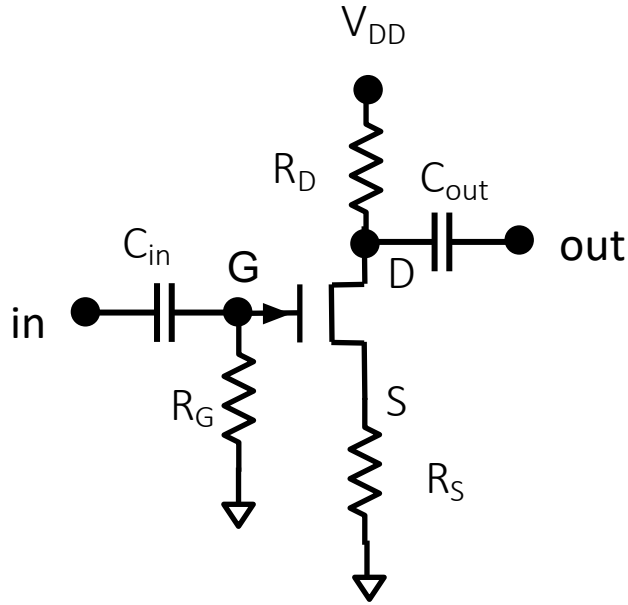


- $A_V = \frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{R_L}, R_S = \frac{-V_P}{i_{dd}} \left(1 - \sqrt{\frac{i_{dd}}{i_{dss}}}\right), g_m \approx 15 \text{ mA/V}$
- 1.  $V_{dd} = 12 \text{ V}, i_{dss} = 35 \text{ mA}, V_P = 3.0 \text{ V}, A_V = 10, i_{dd} = 10 \text{ mA}$
- 2. From eqn above,  $R_S = 139 \Omega, R_D = 10 R_S = 1390 \Omega$
- 3.  $A_V = -g_m (R_D || R_L)$

# Blank


# JFET common drain amplifier

- Similar to BJT emitter follower

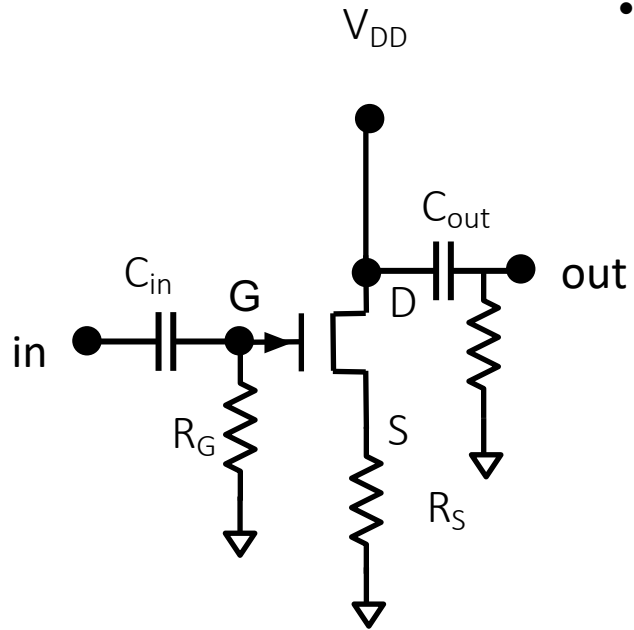

# Blank

# JFET common gate amplifier

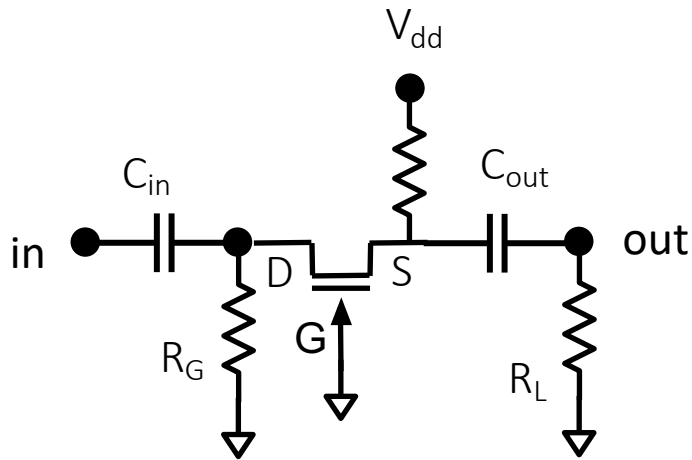

- $V_{DD} = 12V, i_{dss} = 60mA, V_P = -6, A_V = 10, R_L = 1k\Omega, R_S = 50\Omega$

- $i_{d,q} = \frac{V_P}{2R_S^2 i_{dss}} \left( V_P + \sqrt{V_P^2 - 4R_S i_{dss} V_P} \right) - \frac{V_P}{R_S}$


1. Solve for  $R_D$ :  $10 = g_m \times R_D || R_L, R_D = 2k\Omega$

2. Find  $i_{d,q} = \frac{V_P}{2R_S^2 i_{dss}} \left( V_P + \sqrt{V_P^2 - 4R_S i_{dss} V_P} \right) - \frac{V_P}{R_S} = 10mA$

# Blank



# CMOS common emitter amplifier

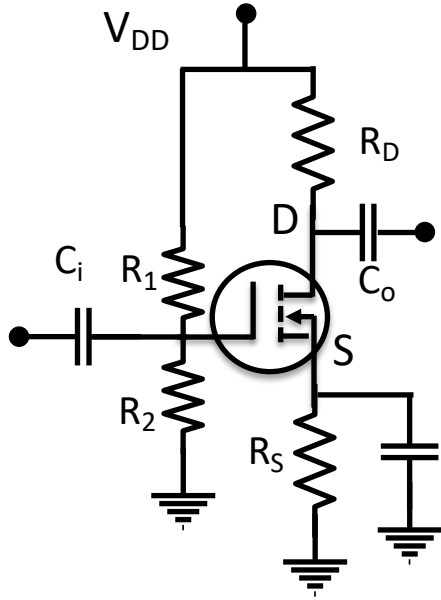


- Pick power
- $V_{DD} = i_D R_D + V_{DS} + i_D R_S$
- $V_{GS} = V_G - i_S R_S$
- $V_G = V_{DD} \frac{R_1}{R_1 + R_2}$
- $i_D = k(V_G - V_{TH})^2$
- Bias around  $\frac{V_{DD}}{3}$
- Pick gain,  $A = \frac{R_D}{R_S + \frac{1}{g_m}}$

# Differential Amplifier


- Two port model
- $\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$
- Pick power  $\overline{\mp}12$
- Choose collector current ( $2mA$ ) by picking  $R_1$
- Pick gain,  $A = \frac{R_C}{2R_E}$

Differential amplifier

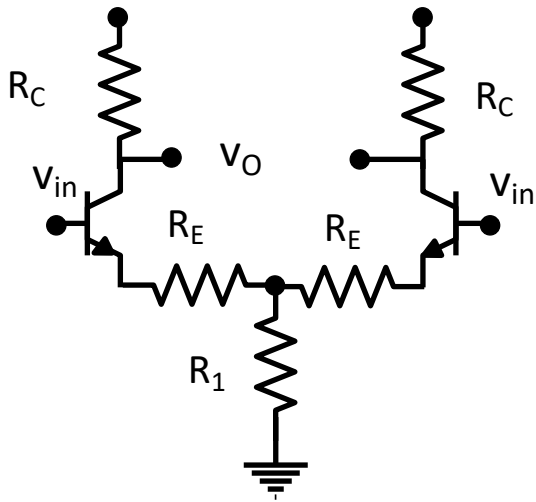


# Exercise 19: Norcal receiver switch

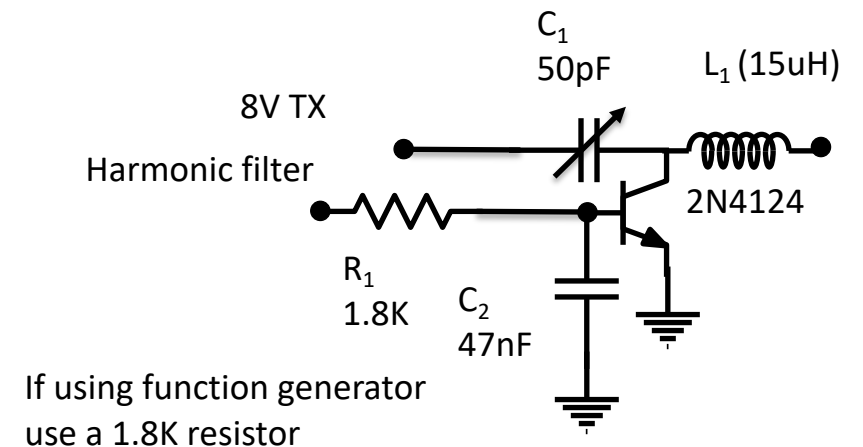1. Consider the rising part of the base voltage waveform. Calculate slope.
2. Do the same for the falling part for voltage below .6V. Calculate  $t_2$ .
3. Measure switch attenuation
4. Measure the voltage with the switch on. Measure output voltage and calculate on-off rejection ratio  $R=20 \log(V_{\text{off}}/V_{\text{on}})$
5. Find the saturation resistance  $R_s$ .
6. Calculate the expected attenuation




# Exercise 20: NorCal transmitter switch

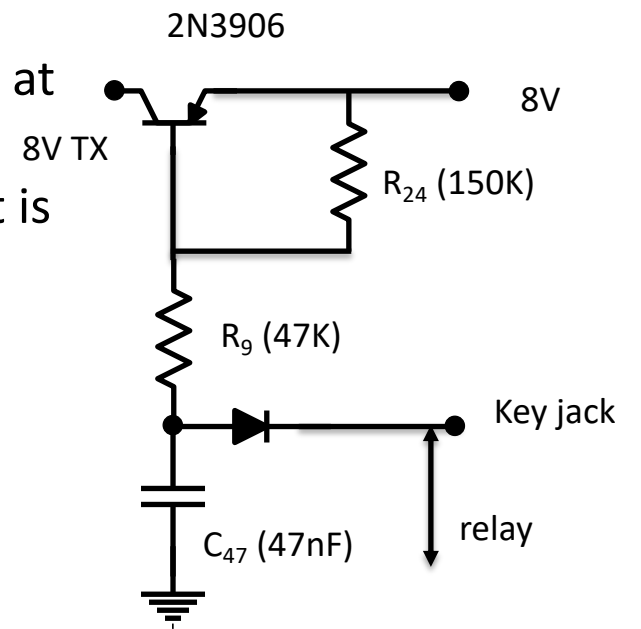1. Calculate voltage on  $C_{57}$ . Measure time for capacitor to charge half-way. Calculate what the time should be.
2. Calculate the approximate current  $i_c$  when Q4 is on. Assume base voltage on Q1 is 700 mV. Neglect saturation voltage on Q4. Calculate base current  $i_b$  required to produce this collector current assuming  $\beta = 100$ .
3. Calculate  $i_b$  at key down assuming a 700 mV drop in base-emitter of Q4 and at 600mV at D11
4. Sketch collector voltage at Q4 showing where transistor is saturated. What is the delay in going active?
5. Use the delay to measure  $\beta$ .




# Exercise 21: Norcal Driver

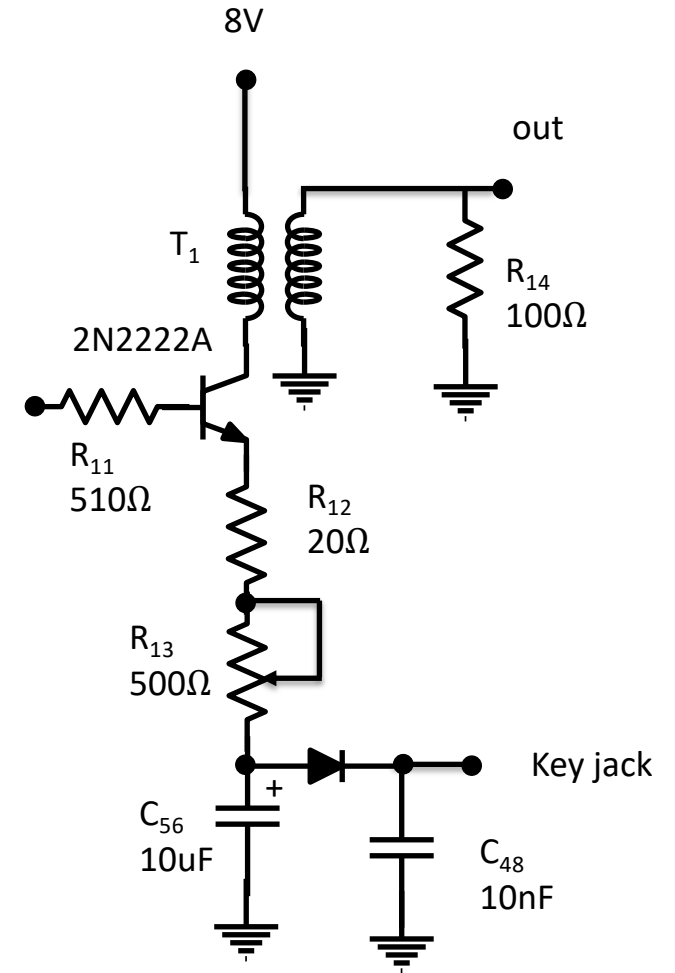1. Measure the voltage gain  $G_v = \frac{v}{v_i}$  with R13 at minimum and maximum gain.
2. Calculate expected voltage gain at each setting.
3. 560ohm source resistance  $V_o = 2V$




# Emitter degeneration

- To the usual transistor circuit (A), on the right, we add  $R_E$ . (B) is an equivalent circuit.
- $V_{bb} \approx V_f + i_c R_E$ . Let  $V$  be the output AC and  $V_i$  be the input AC, then the gain is  $G = \frac{V}{V_i}$ .
- $V_i = i_b r_b + i_E R_E \approx i_c R_E$ ,  $Z_i = \frac{V_i}{i_b}$ ,
- $V = -i_c R_C$ . So  $G_v = -\frac{R_C}{R_E}$  (Doesn't depend on  $\beta$ ).
- $V_i \approx \beta i_b R_E$  and  $Z_i = \frac{V_i}{i_b}$ , so  $Z_i = \beta R_E$ .
- $C_M$  is called a Miller capacitor,  $i_m = j\omega(V_i - V) = j\omega C_M(1 + |G_v|)V_i$
- So with the Miller capacitor,  $Z_i = \beta R_E || (1 + |G_v|)C_M$
- $r_c \approx \frac{V_{early}}{i_c}$ ,  $r_c$  is the collector resistance
- $R_s' = R_s + r_b$ ,  $r_b$  is the base resistance
- $z_c = r_c || C_c$ ,  $C_c$  is specified in data sheet (8pF),  $z_c$  is the collector impedance
- $Z_o = \frac{V}{i_c}$ ,  $i = i_c - \beta i_b$ ,  $i_b = -\frac{i_c R_s}{R_s' + R_E}$ ,  $i = i_c(1 + \frac{\beta R_E}{R_s' + R_E})$
- $V = i z_c + i_c (R_s' || R_E)$
- $Z_o = \frac{V}{i_c} = z_c \left(1 + \frac{\beta R_E}{R_s' + R_E}\right) + R_s' || R_E$ .
- $|z_c| \gg R_E$ , so  $Z_o = z_c \left(1 + \frac{\beta R_E}{R_s' + R_E}\right)$

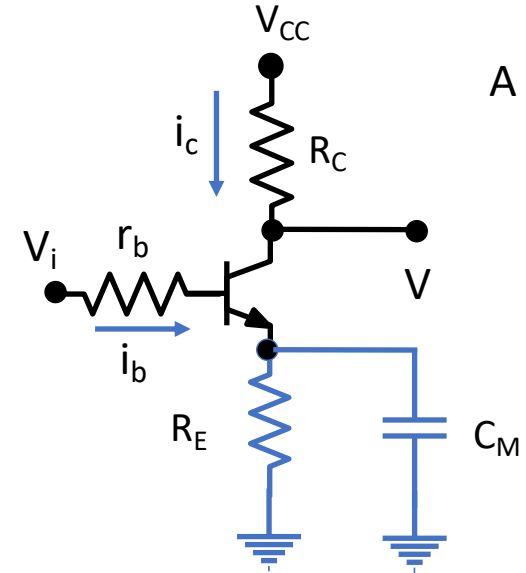

Adding  $R_E$  (and  $(C_M)$ )

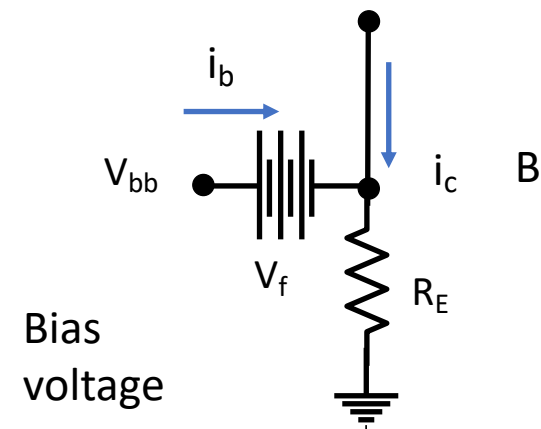


Bias voltage

# Exercise 22: Emitter degeneration

- In Driver amplifier, add probe to  $R_{11}$ , this allows us to measure the AC voltage,  $V_i$ 
  1. Measure  $G_v = \frac{V}{V_i}$  with  $R_{13}$  turned fully counterclockwise
  2. Calculate the expected voltage gain for each setting
  3. Measure  $V_i$  at the maximal gain setting
  4. The open circuit voltage is  $V_0 = 2V$ , calculate  $V_i$  in terms of  $C_M$

# Exercise 23: Norcal Buffer amplifier

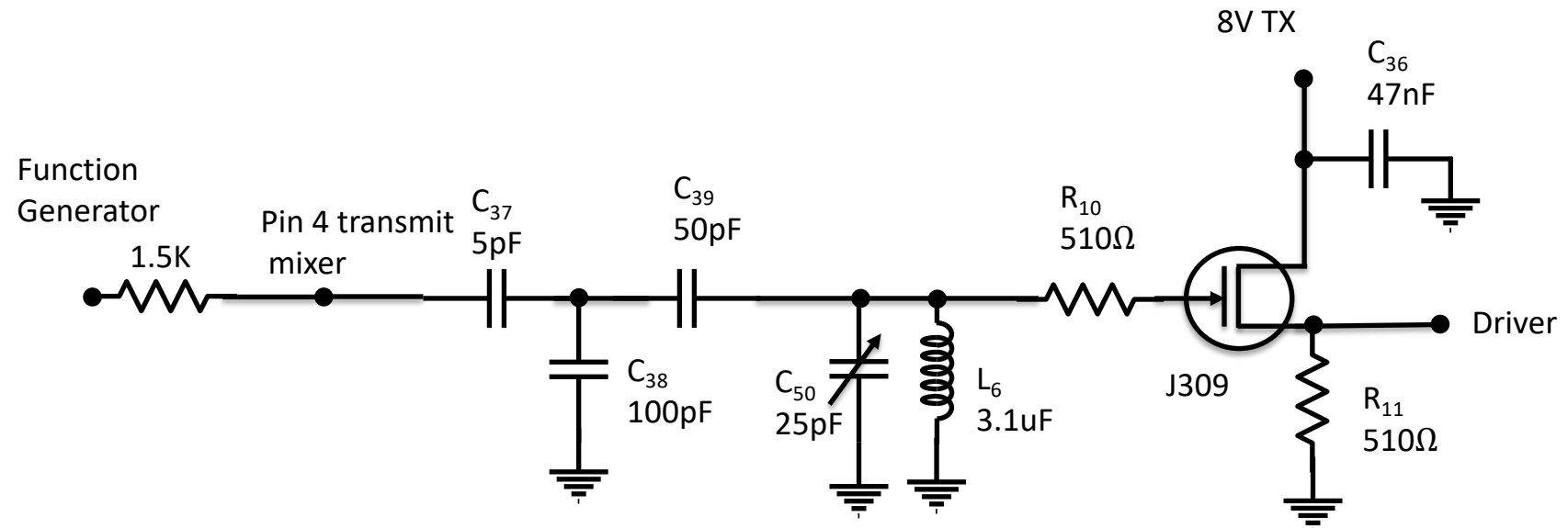1. Measure the DC voltage at source of the JFET
2. Calculate the source and drain voltages you should expect
3. Measure the voltage gain
4. Find the transconductance you should expect
5. Calculate the available power  $P_+$  from the function generator through a 1.5Kohm load. Calculate gain in dB











# Amplifier classes

Class	Efficiency	Characteristics
A	35%	Full bias
B	60%	Low bias
C	75%	Saturating
D	75%	Switch in pass-band
E	90%	Voltage switch
F	80%	Harmonic resonators


$$\eta = \frac{P}{P_0}, P_d = P_0 - P_i$$

$$P_d = P_a + P_{on}$$

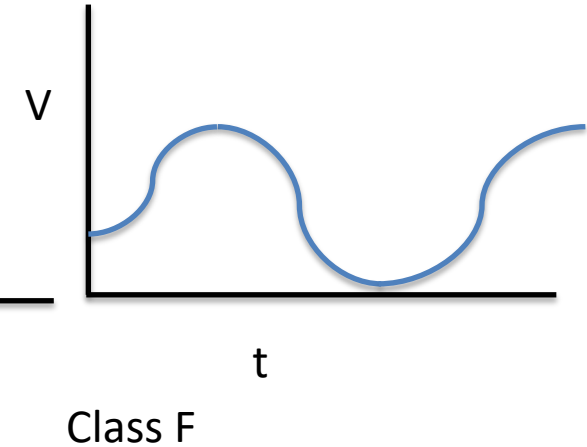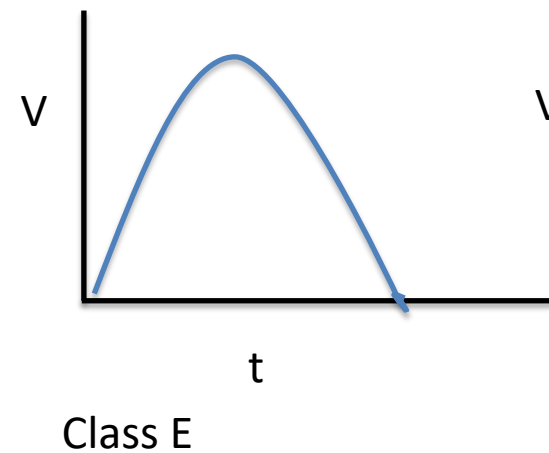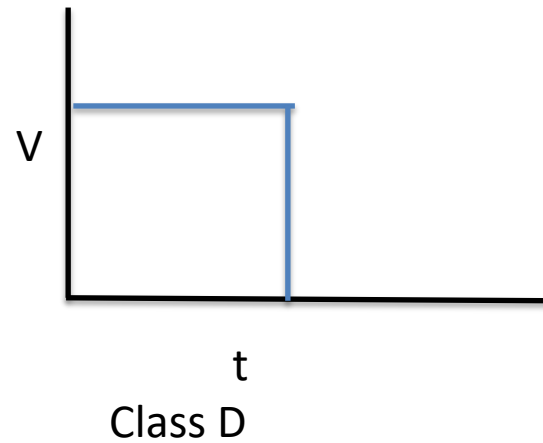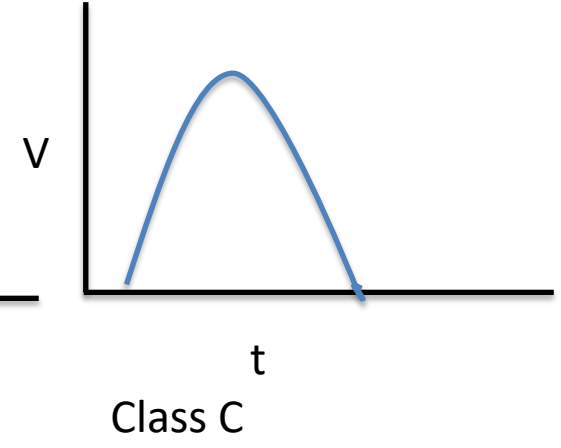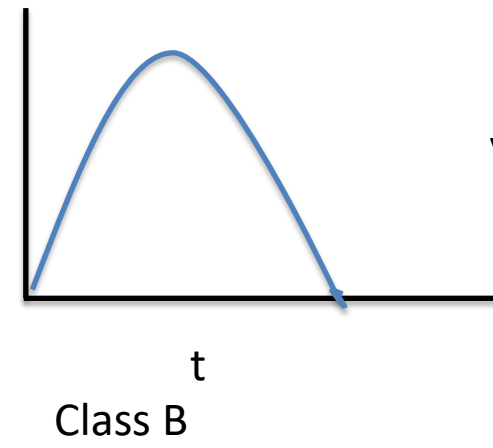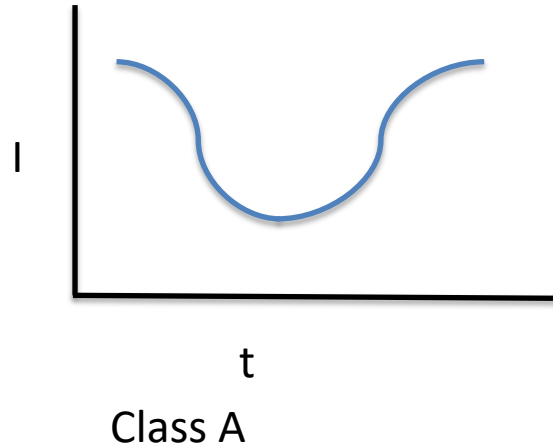


# Exercise 24: Norcal Power Amp

Norcal-40 Power amp is class C

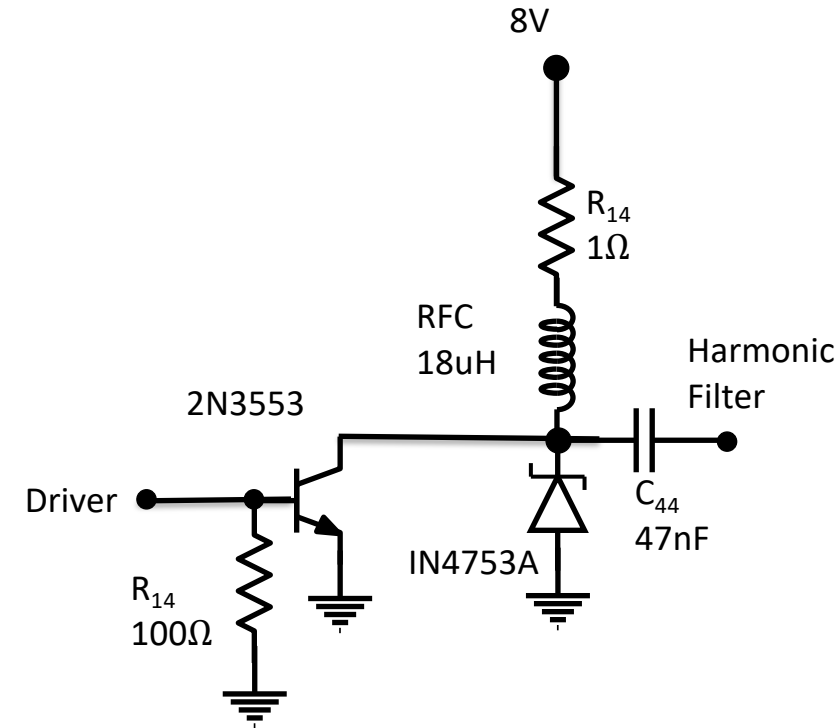

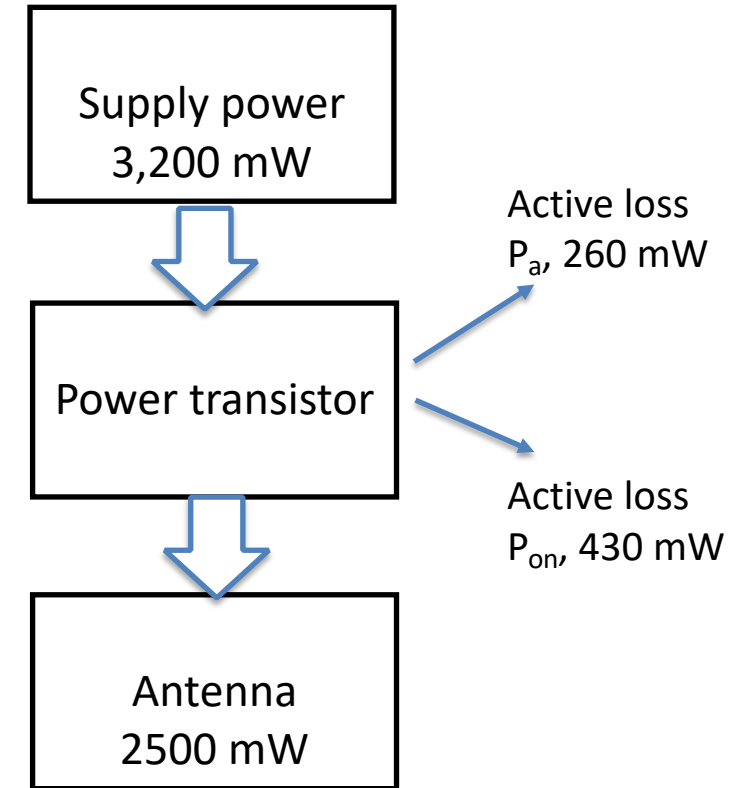- $R_t = \frac{T - T_0}{P_d}$
  - $T_0$  is ambient temperature,  $T$  is heat sink temperature Type equation here.
1. Calculate pp across 50ohm load required for output of 2W
  2. Find pp output voltages or 5, 10, 15, 20, 25 and 30V. Calculate power supply current subtracting 2mA for regulator
  3. Plot efficiency  $\eta = \frac{P_o}{P_i}$ . Plot dissipated power  $P_d = P_o - P_i$



# Thermal modelling


- $T$  is heat sink temperature,  $T_0$  is ambient temperature,  $P_d$  is power dissipated.
- $R_t = \frac{T - T_0}{P_d}$ ,  $R_t$  is the thermal resistance
- $C_t \dot{T} = P_d$ ,  $C_t$  is the thermal capacitance
- $R_j = \frac{T_j - T}{P_d}$ ,  $T_j$  is the junction temperature
- $f(t) + \tau \dot{f}(t) = f_\infty$ ,  $f(t) = f_0 e^{-\frac{t}{\tau}}$
- $P_d = \frac{T(t) - T_0}{R_t} + C_t T \dot{(t)}$ ,  $\tau = C_t R_t$ ,  $T_\infty = P_d R_t + T_0$
- $T(t) + \tau \dot{T}(t) = T_\infty$ ,  $\tau = C_t R_t$ .
- $T_\infty = P_d R_t + T_0$
- $T(t) = T_\infty - P_d R_t e^{-\frac{t}{\tau}}$
- $T_j(t) = T(t) + R_j P_d$

# Exercise 25: Thermal modelling

- x


# Clapp oscillator

- $i_d = g_m v_{gs}$
- Resonance:  $-\frac{1}{j\omega_0 C_2} = j\omega_0 L + \frac{1}{j\omega_0 C_3} + \frac{1}{j\omega_0 C_1}$
- $\omega_0 = \frac{1}{\sqrt{LC}}, C = C_1 || C_2 || C_3$
- At resonance,  $v_{gs} = R i_d \frac{C_1}{C_2}, L = \frac{C_1}{RC_2}$
- Oscillation continues if  $g_m > \frac{C_1}{RC_2}$
- $v_{gs} = 2v_s$

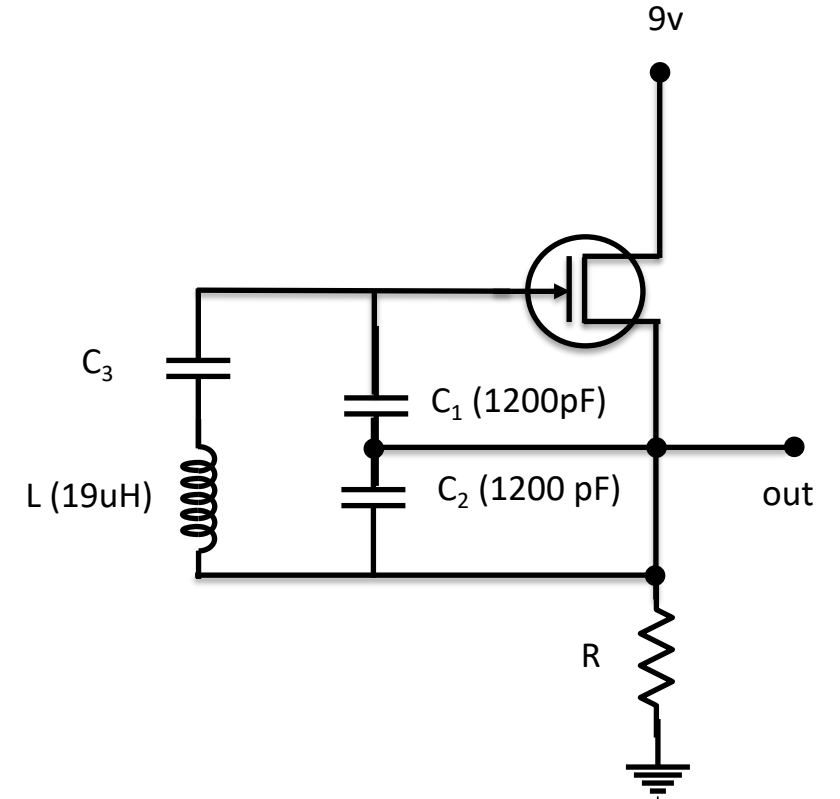

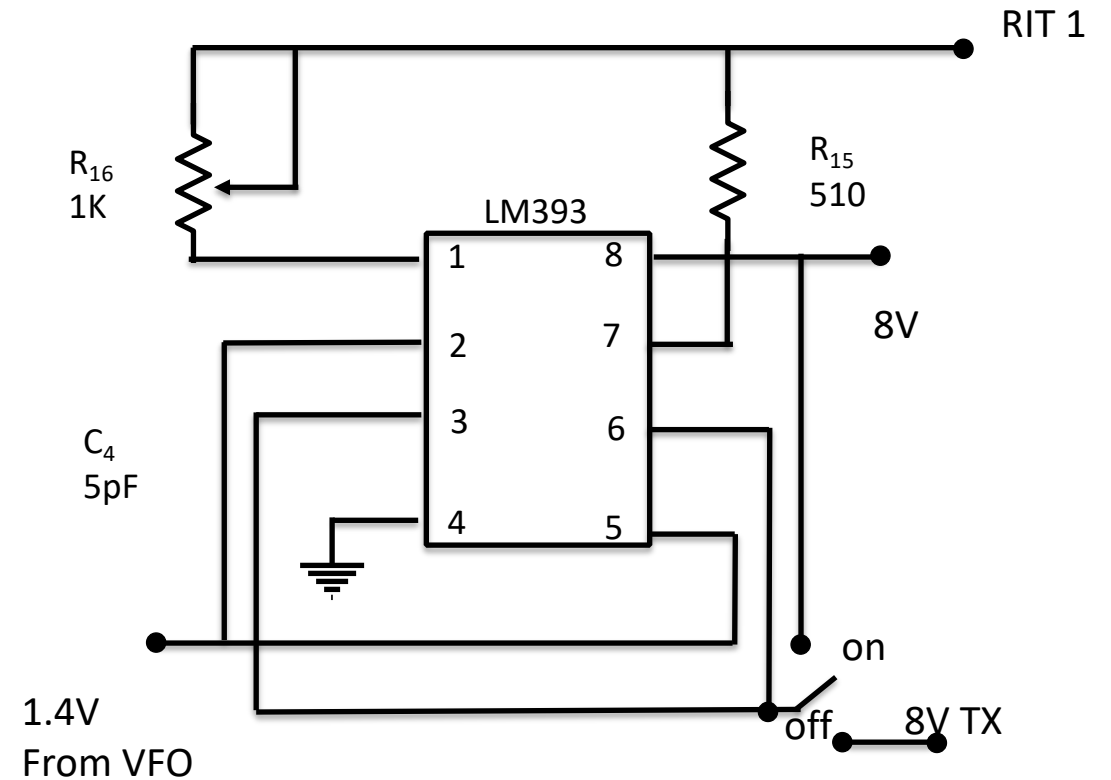
# Norcal Receiver Incremental Tuning (RIT)

- LM393 is a comparator
- For function generator connect through 1.5K



# Exercise 26: Norcal VFO

- L9: T68-7 62 turns
  - Check MVAM108 capacitor when  $R_{17}$  is high and low
  - Start resistor ( $R_{21}$ ) pulls gate to ground at start
  - When gain limiting diode ( $D_9$ ) conducts, it pulls gate negative
  - Oscillator keeps growing as long as  $g_m > 1/R$
1. Measure DC voltage across wiper in  $R_{17}$
  2. Calculate expected  $V$  for large signal oscillation
  3. How does this change if we consider the inductor and source-drain resistance
  4. How does the frequency change as  $R_{17}$  changes?
  5. Calculate the oscillation frequency and the loss ratio  $|V/V_i|$

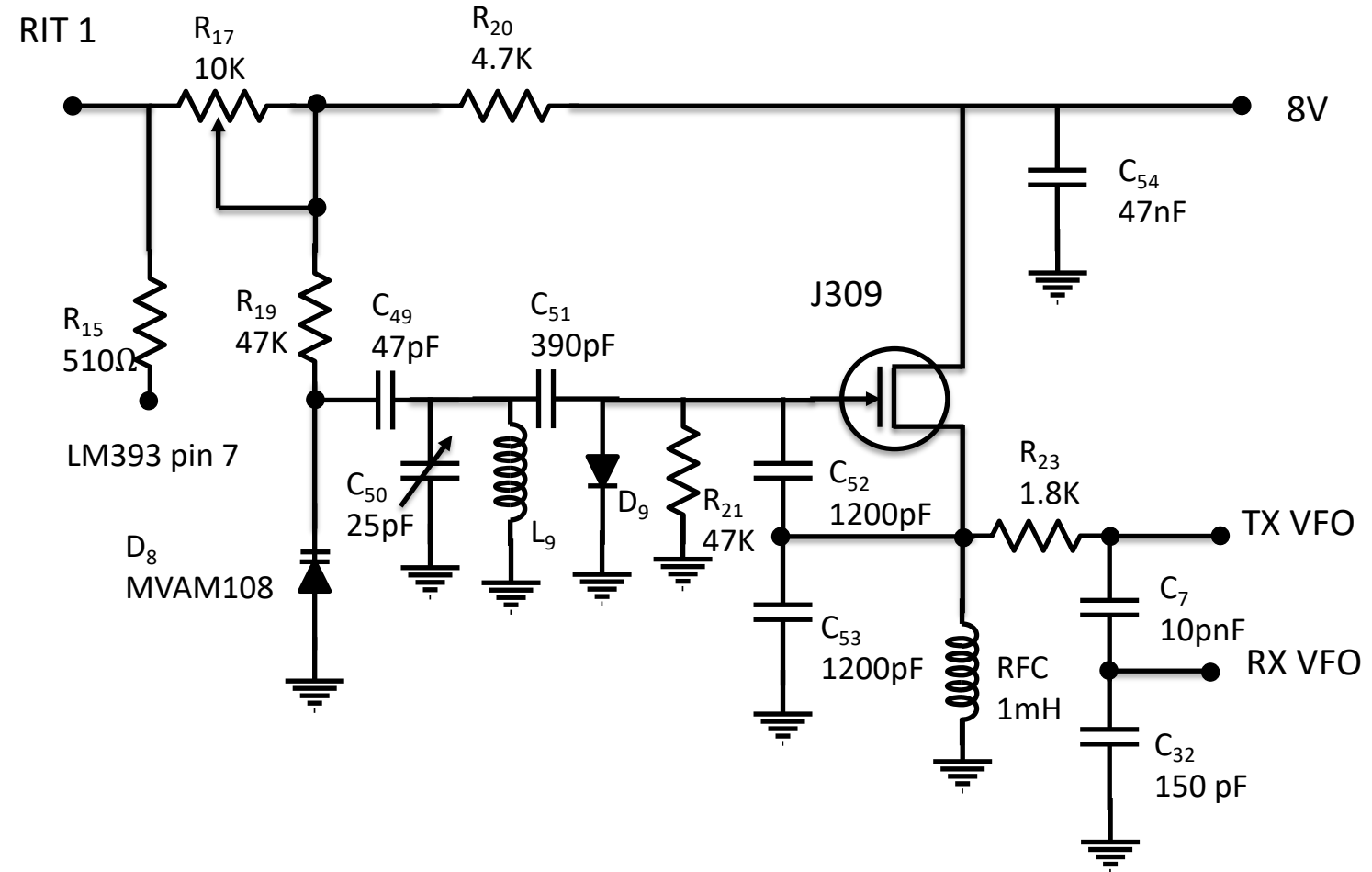

# Exercise 27: Gain limiting

- $x$




# Mixers

- $x$


# Exercise 28: Norcal RF Mixer

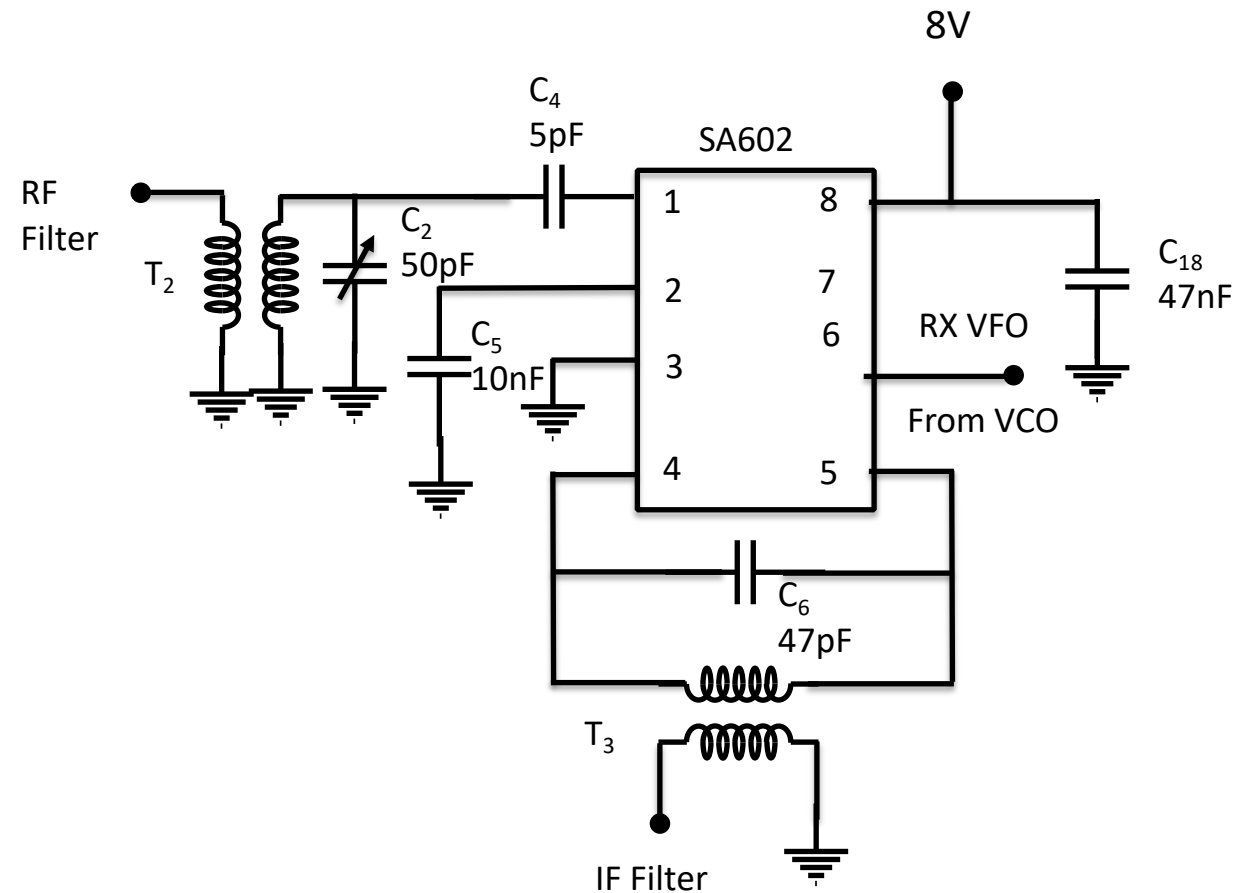1. Measure conversion gain of the Mixer.
2. How much attenuation is provided by pot?
3. By how many dB is the image response suppressed



# Exercise 29: Norcal Product Detector

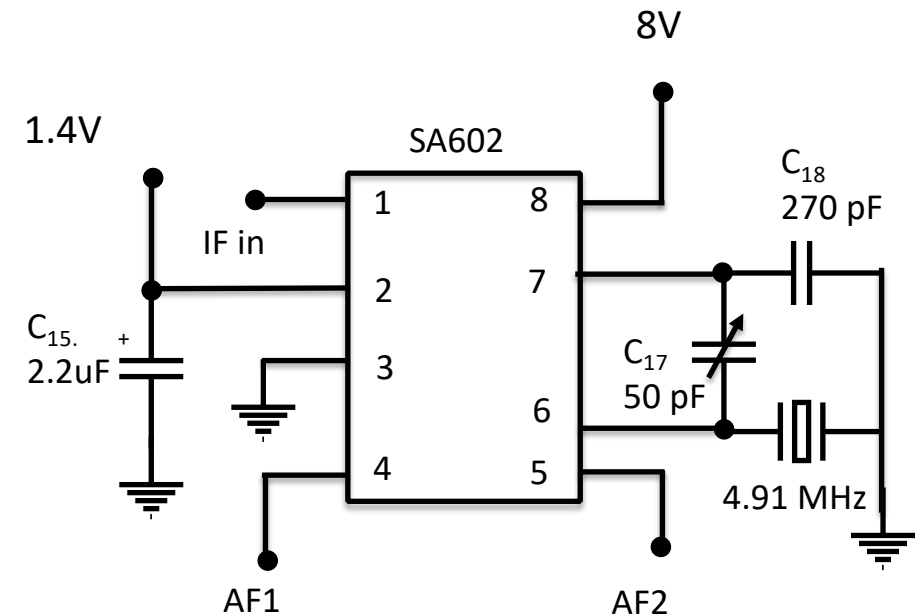
1. Adjust C17 for minimum oscillation frequency and record it
2. Calculate the minimum oscillation frequency you'd expect
3. Measure the temperature coefficient for the BFO
4. Measure the gain through the receiver from the antenna through the product detector
5. Find the f5 spur calculate the expected f3
6. By how much is the if spur suppressed



- 620 Hz output through AF1 and AF2


# Exercise 30: Norcal transmit mixer and oscillator

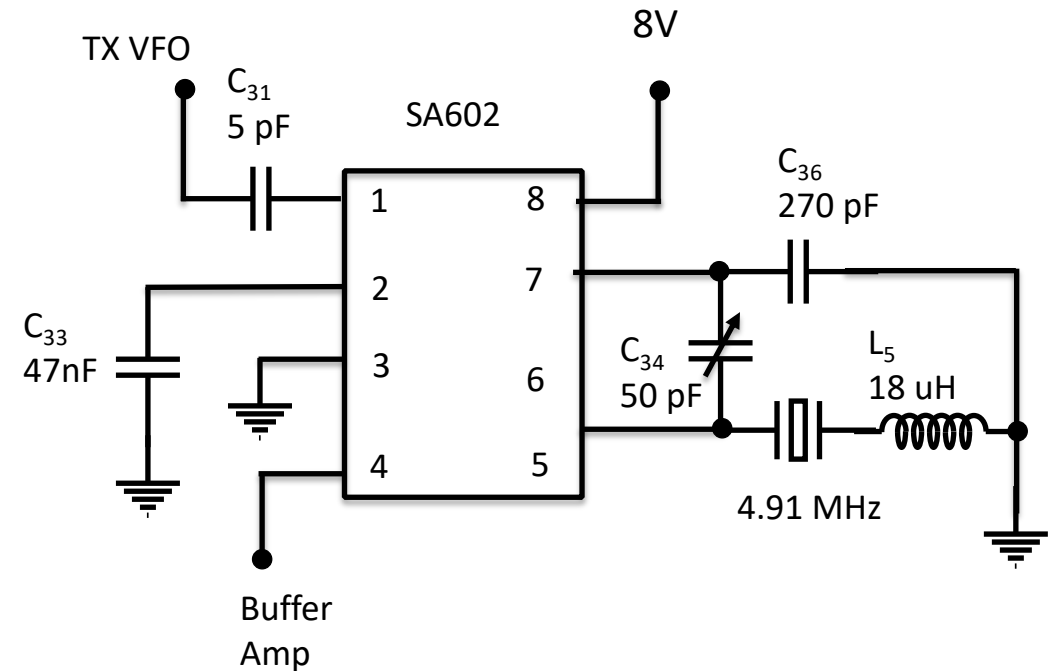1. How much would you expect the inductor to lower the oscillation frequency
2. Use the TX VFO and the voltage attenuation to calculate the input power from the transmit mixer. Calculate the gain through the entire chain
3. Measure the rise and fall time of keying response
4. There is a spurious  $f_{mn} = mf_{vfo} + nf_{to}$ .




# Exercise 31: Norcal Audio Amp

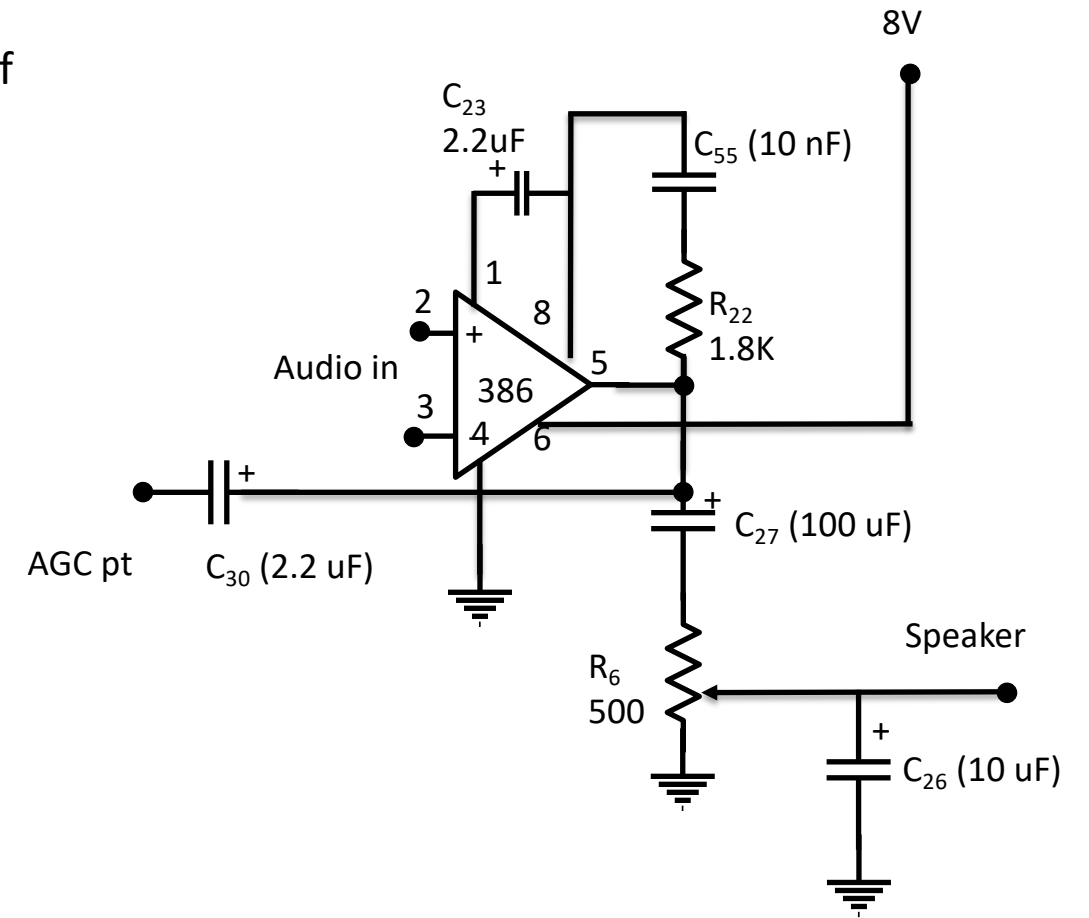1. Calculate input  $V_i$  assuming very high input impedance
2. Measure the voltage gain  $G_v$  at high frequency and 3dB rolloff



# Exercise 32: Norcal AGC

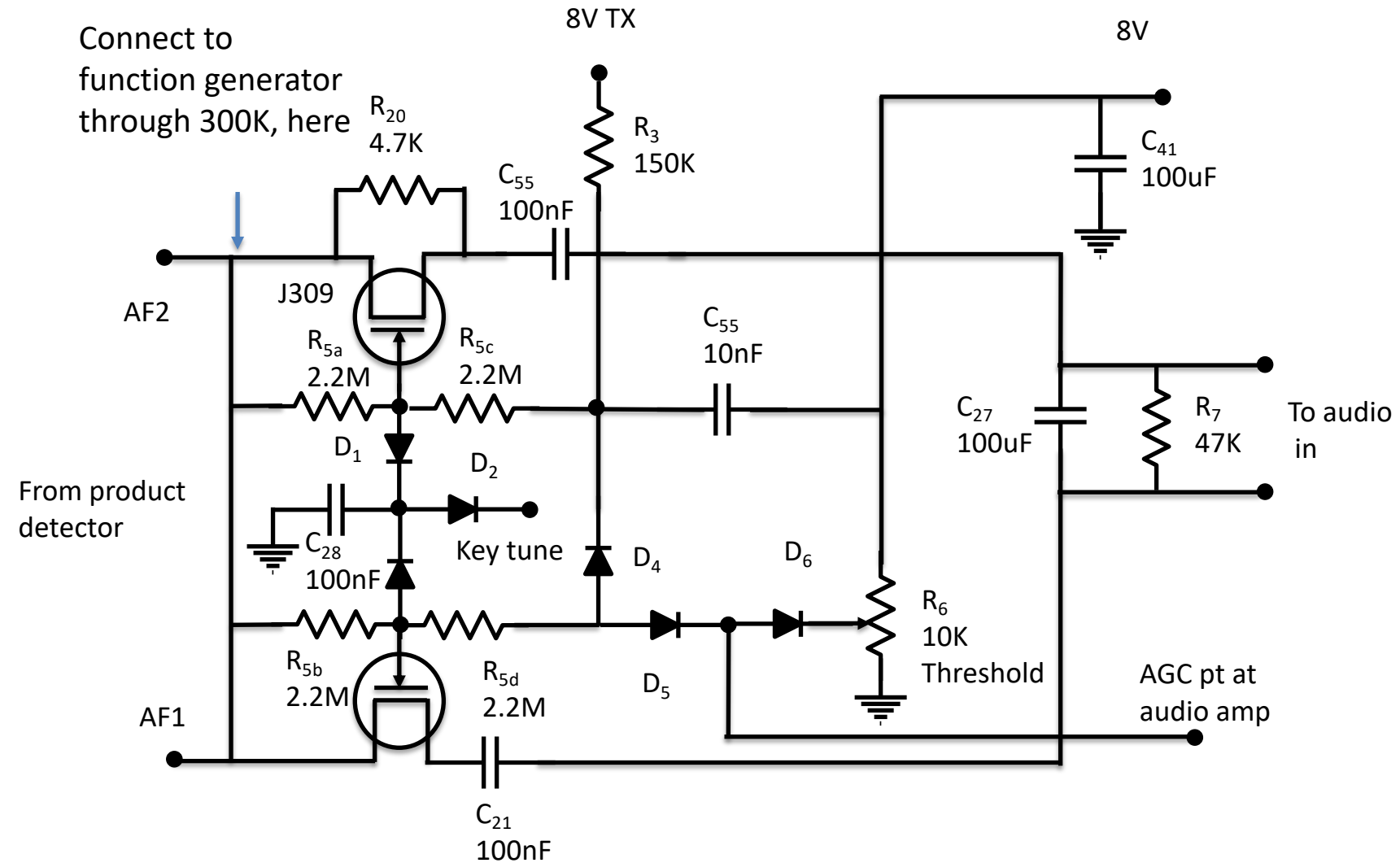


# Exercise 33: Alignment

- $x$

# Antennas and propagation

- From Maxwell, for a plane wave (E in x direction, H in y direction), wave is of form  $\exp(j\omega t - j\beta z)$
- $\nabla \times E = -j\mu_0\omega H$
- $\nabla \times B = j\epsilon_0\omega E$
- $\beta \hat{z} \times E = \mu_0\omega H, \beta E_x \hat{y} = \mu_0\omega H$
- Substituting and taking the restricted cross products, we get:  $\beta E_x = \omega\mu_0 \frac{\omega\epsilon_0}{\beta}$ , so  $\beta = \omega\sqrt{\mu_0\epsilon_0}$
- Power density:  $S = \text{Re} \left( \frac{E_x \overline{H_y}}{2} \right) = \frac{(|E_x|)^2}{2\eta_0}$
- $\eta_0 = \frac{E_x}{H_y} = \sqrt{\frac{\mu_0}{\epsilon_0}} = 377\Omega$
- Impedance:  $P_t = \frac{R|I|^2}{2}$ , R is real part of Z,  $R = R_r + R_l, \eta = \frac{R_r}{R}$
- Power density for isotropic antenna:  $S_i = \frac{P_t}{4\pi r^2}$
- Define  $G(\theta, \phi) = \frac{S(\theta, \phi)}{S_r}$ .  $S(\theta, \phi)$  is just the Poynting vector
- For isotropic reference,  $G = \frac{4\pi r^2 S}{P_t}$

Receiving antenna Thevenin

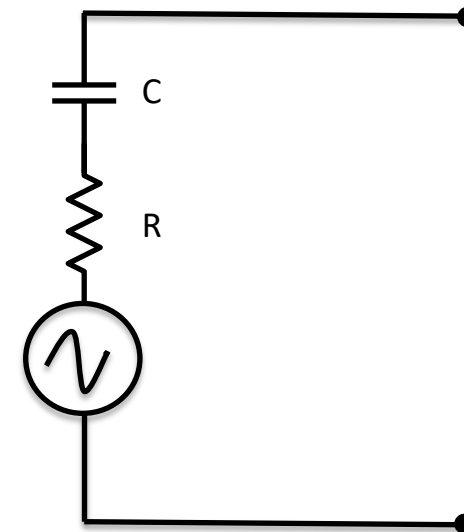




# Antennas and propagation

- Receiving antenna:
- $V_0 = hE$ ,  $h$  is effective antenna length ( $h = \frac{l}{2}$  for short antenna)
- For dipole:  $V_0 = \frac{l}{2} E \sin(\theta)$
- $A(\theta, \phi) = \frac{P_r}{S(\theta, \phi)}$ . This is the definition of the effective area,  $A$ .
- By reciprocity,  $A(\theta, \phi) = \frac{\lambda^2}{4\pi} G(\theta, \phi)$
- $P_r = \frac{|V_0|^2}{8R_a} = \frac{|hE|^2}{8R_a}$ , so
- $P_r = \frac{h^2 S \eta_0}{4R}$
- $A = \frac{h^2 \eta_0}{4R}$

# Antennas and propagation

- Antenna theorem:  $\oint A d\Omega = \lambda^2$
- For cavity on right, T is constant at thermodynamic equilibrium and the same power is transmitted and emitted, the Johnson noise is  $kT$ . The energy received is  $E = \frac{4\pi kT}{c\lambda^2}$ . Set  $B = \frac{kT}{\lambda^2}$ .  $kT = \oint BA d\Omega = \oint A \frac{kT}{\lambda^2} d\Omega$ , which gives the antenna theorem
- For transmitting/receiving antenna pairs:  $G_1 A_2 = \frac{|V|^2 \pi r^2}{|I|^2 R_1 R_2} = G_2 A_1$ . So  $\frac{G_1}{A_1} = \frac{G_2}{A_2} = \frac{4\pi}{\lambda^2}$
- Friis formulas
- $S = \frac{P_t G}{4\pi r^2}, P_r = SA = \frac{P_t G A}{4\pi r^2}$


Insulated cavity

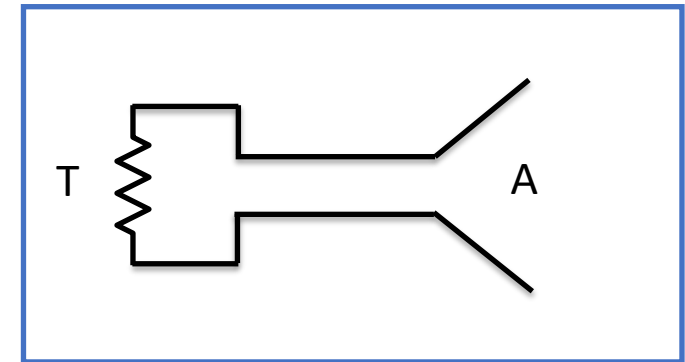

# Reciprocity and dipole

- For dipole (Length:  $l = \frac{\lambda}{2}$ )
- $\lambda^2 = \int A d\Omega = \int \frac{h^2 \eta_0}{4R_r} d\Omega$ , so
- $R_r = \frac{l^2 \eta_0}{16\lambda^2} \int \sin^2(\theta) d\Omega = \eta_0 \frac{\pi}{6} \left(\frac{l}{\lambda}\right)^2$
- $A = \frac{3\lambda^2}{8\pi} \sin^2(\theta)$  and  $G = 1.5 \sin^2(\theta)$ . . Note we used  $h = \frac{l}{2} \sin(\theta)$
- For Norcal,  $G = 1$ ,  $A = 150 \text{ m}^2$ , for  $r = 2000 \text{ m}$ ,  $P_r = 6 \text{ pW}$

Dipole Thevenin equivalent circuit

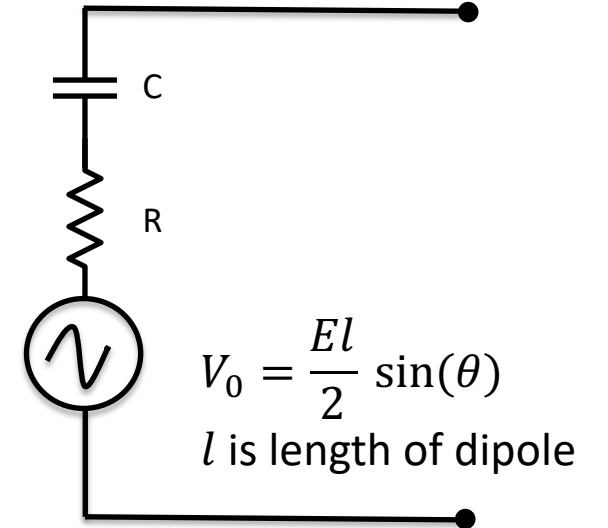

# Noise

- $V_{n(rms)} = \sqrt{\frac{1}{\tau} \int_0^\tau V(t)^2 dt}$
- $P_n = \frac{V_{n(rms)}^2}{R}$ ,  $R$  is load resistance
- $SNR = \frac{P}{P_n}$
- $MDS = \frac{P_n}{G}$
- Nyquist
- $V_C = \frac{1}{j\omega C} \frac{V_n}{R + j\omega L + \frac{1}{j\omega C}}$
- $\overline{|V_C|^2} = \frac{\overline{|V_n|^2}}{|1 - \omega^2 LC + j\omega RC|^2}$
- Expected energy at resonance is  $kT = \frac{C}{2} \int_0^\infty |V_C|^2 df$
- $\int_0^\infty \frac{1}{|1 - \omega^2 LC + j\omega RC|^2} df = \frac{1}{4RC}$
- So,  $\overline{|V_C|^2} = 8kTR$

# Exercise 35: Intermodulation

1. Find coefficients and frequencies for  $[\cos(\omega_1 t) + [\cos(\omega_2 t)]^5]$


# Exercise 37: Antennas

1. Use the relation between gain and effective area to rewrite the Friis transmission formula in terms of gain only. Consider UHF for airplanes. If the frequency makes the quarter length stub antenna have gain 2, find the maximum possible LOS at 10km height. Required receiver power is  $-100$  dBm. Find the minimum transmission power.
2. Find the inductance to resonate with a 3m whip. Assuming the Q of the coil is 200, find the turns ratio required to give a transceiver a 50 ohm load. What is the radiation efficiency?
3. Repeat 2 with a capacitive end loading, assuming the capacitance doubles.

# Exercise 38: Propagation


- $x$

# Norcal circuit diagram, 1

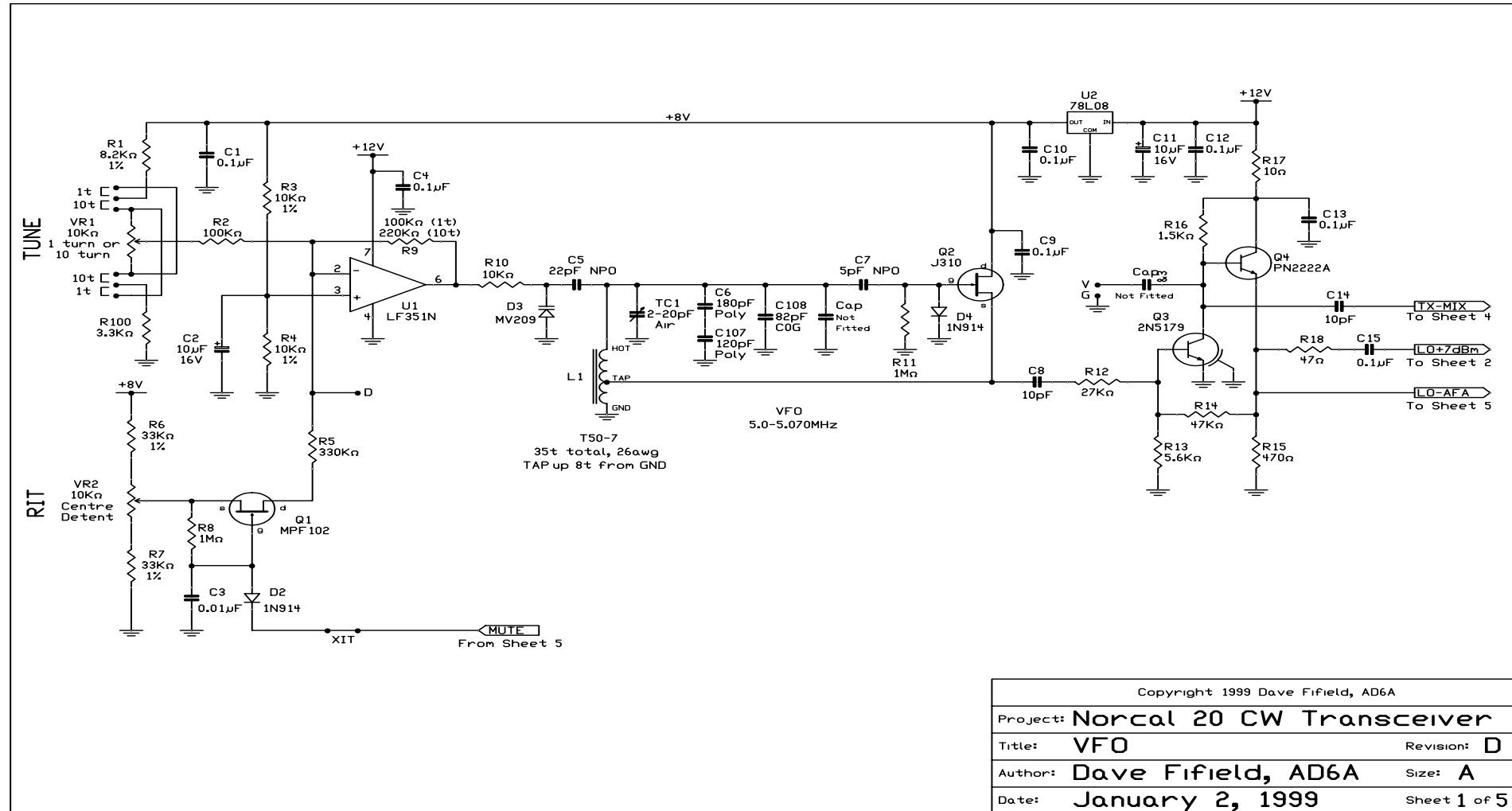





# Norcal circuit diagram, 2

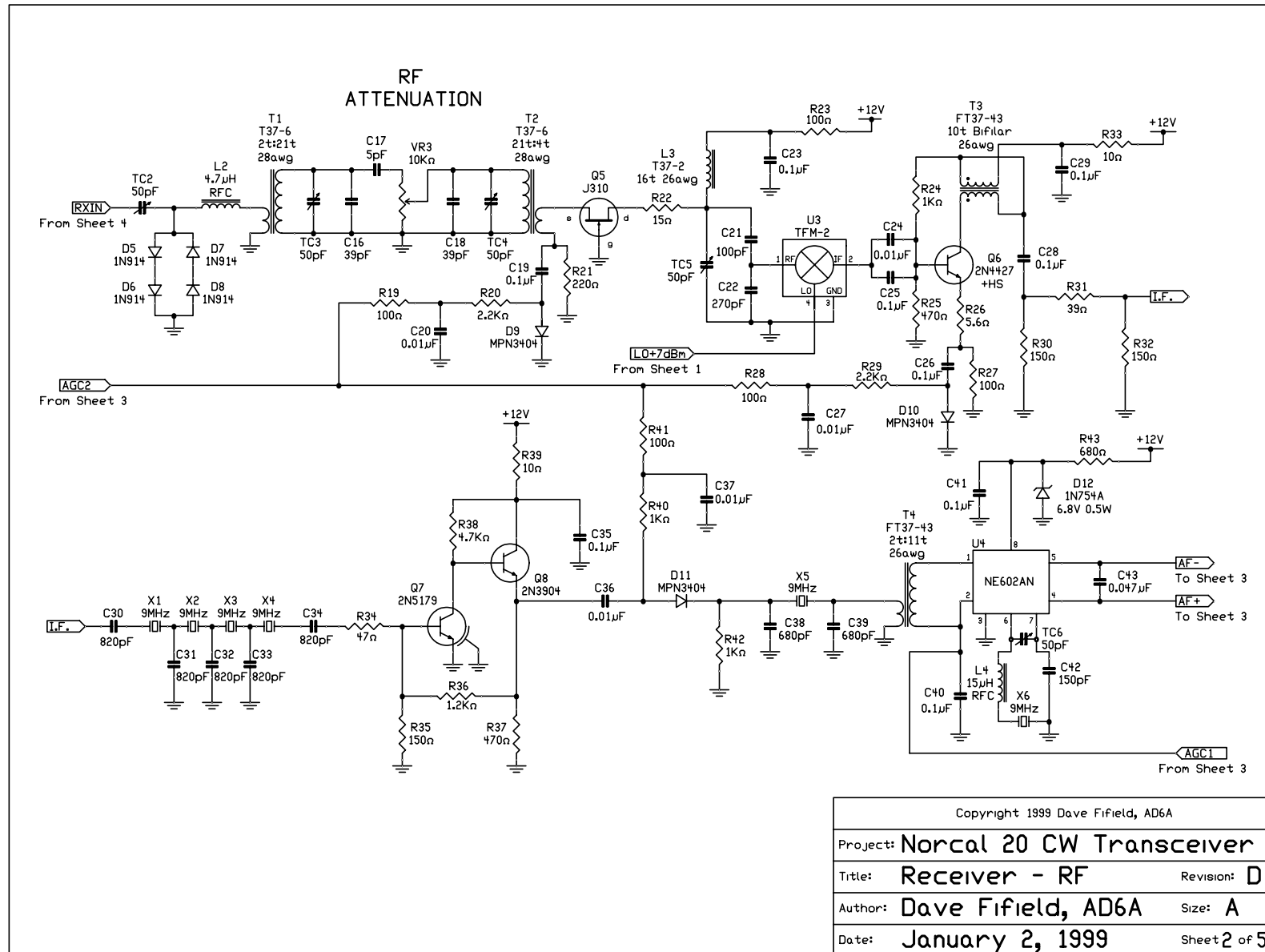


# Norcal circuit diagram, 3

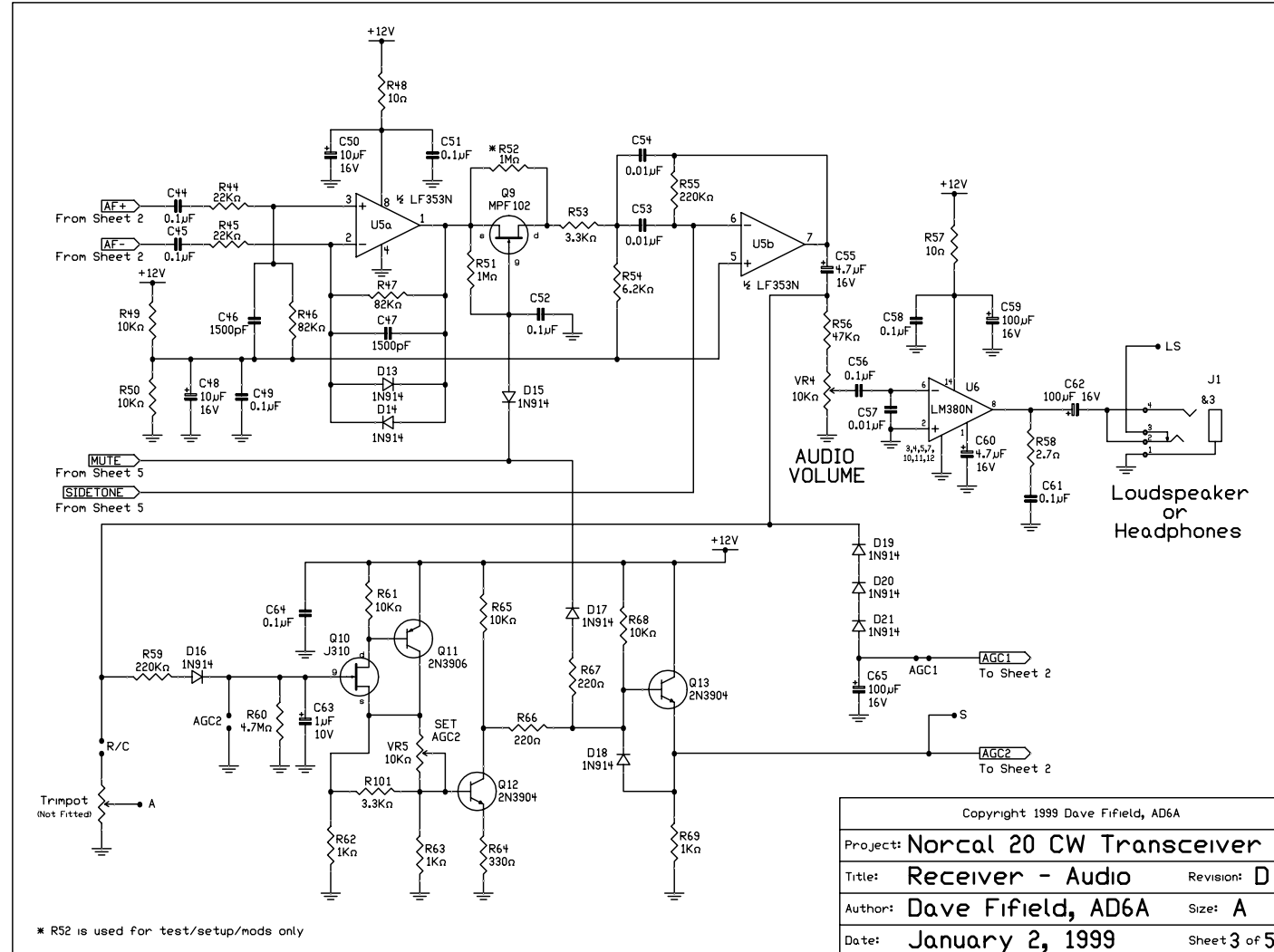

# Norcal circuit diagram, 4

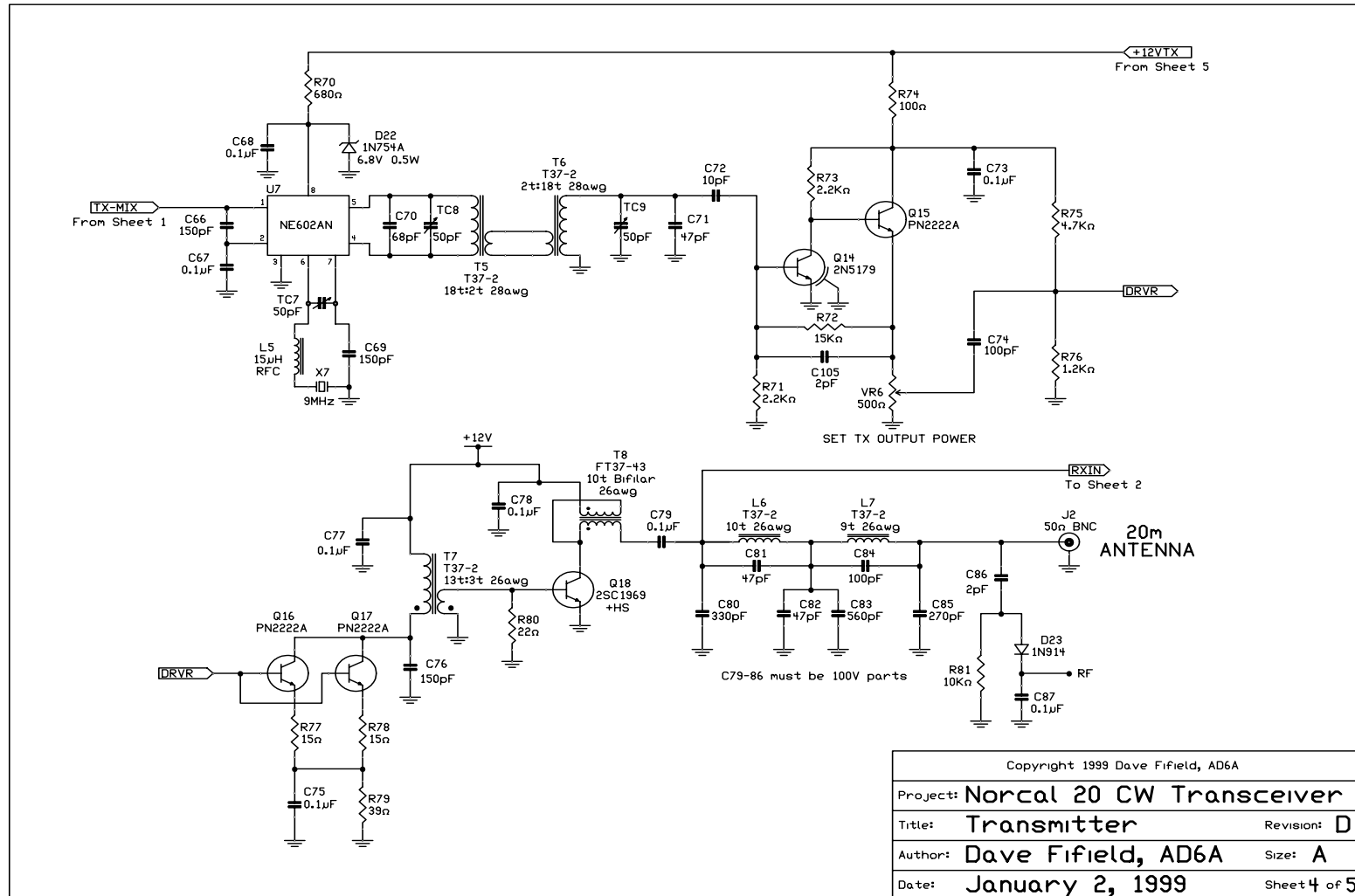

# Norcal circuit diagram, 5

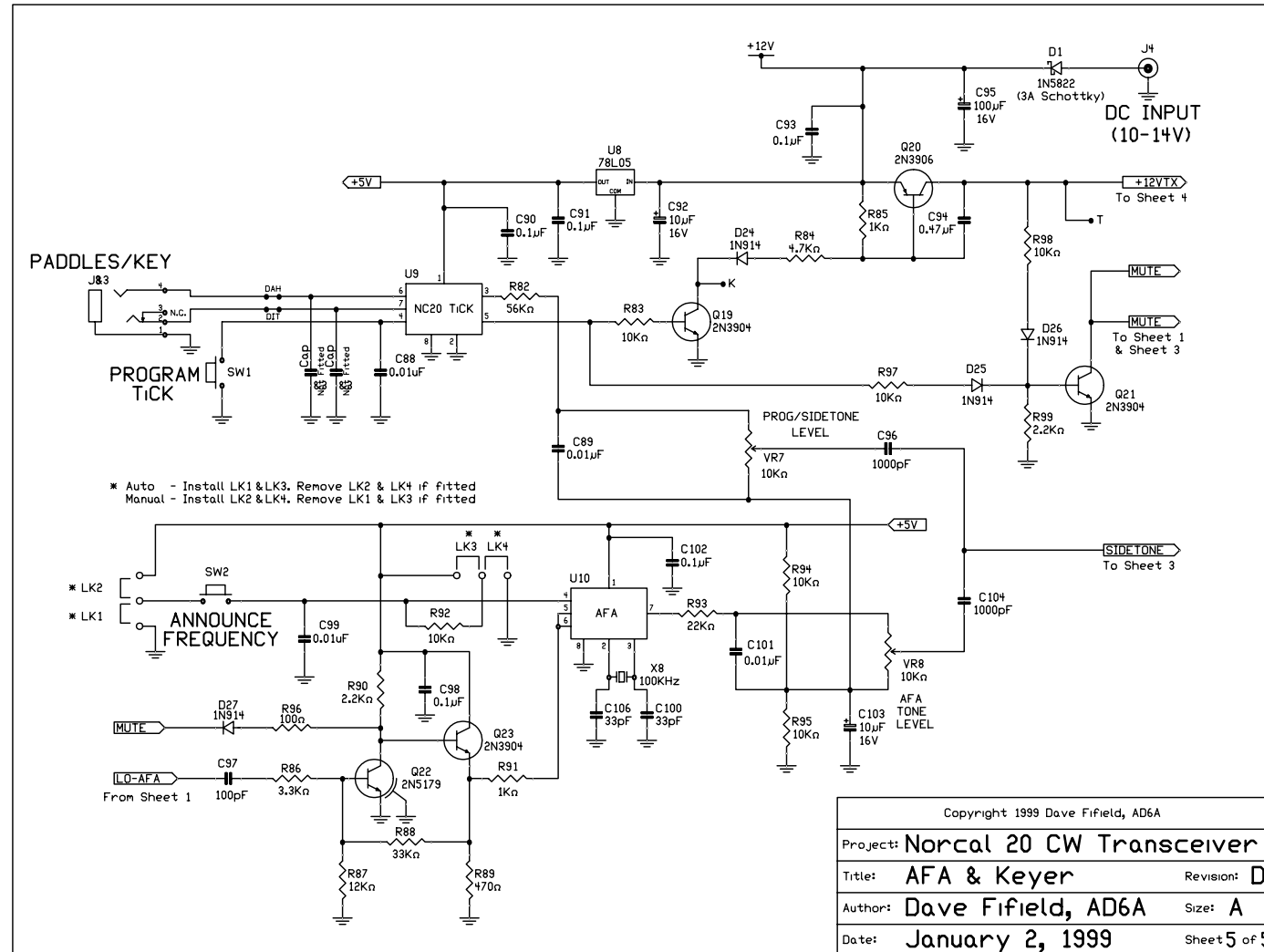


# Morse


Symbol	Code	Symbol	Code	Symbol	Code
a	._	m	__	y	_.
b	__...	n	_.	z	__..
c	_.	o	___	0	_____
d	_.	p	_.	1	_.
e	.	q	___.	2	..
f	..	r	_.	3	..._
g	__.	s	...	4	...._
h	....	t	_	5	.....
i	..	u	..	6	_....
j	_.	v	..._	7	__...
k	_.	w	_.	8	____..
l	_.	x	_.	9	____.

# Color codes

## RESISTOR COLOR CODE GUIDE

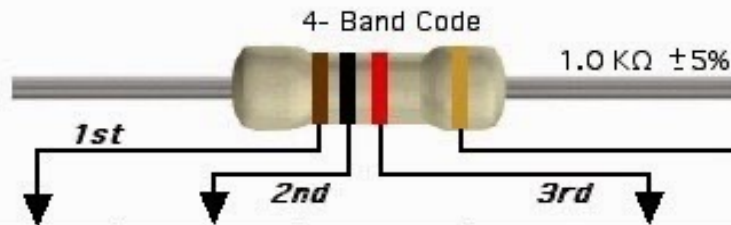

Color	1st Band	2nd Band	3rd Band	Decimal Multiplier		Tolerance
Black	0	0	0	1	1	
Brown	1	1	1	10	10	$\pm$ 1 %
Red	2	2	2	100	100	$\pm$ 2 %
Orange	3	3	3	1K	1,000	
Yellow	4	4	4	10K	10,000	
Green	5	5	5	100K	100,000	
Blue	6	6	6	1M	1,000,000	
Violet	7	7	7	10M	10,000,000	
Gray	8	8	8	100,000,000		
White	9	9	9	1,000,000,000		
Gold				0.1		$\pm$ 5 %
Silver				0.01		$\pm$ 10 %
None						$\pm$ 20 %

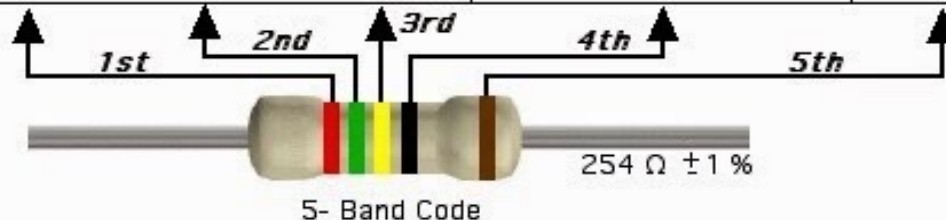

- Resistors: ohms
- Capacitors: picoFards
- Inductors: milliHenries